

Problem

In an electric circuit, the dual of resistance is:

- a) conductance
- (b) inductance
- (c) capacitance
- (d) open circuit
- (e) short circuit

Step-by-step solution**Step 1** of 5

Refer to table 8.1 in the textbook.

The dual of inductance is capacitance. Hence, option (b) is incorrect.

Step 2 of 5

The dual of capacitance is inductance. Hence, option (c) is incorrect.

Step 3 of 5

The dual of open circuit is short circuit. Hence, option (d) is incorrect.

Step 4 of 5

The dual of short circuit is open circuit. Hence, option (e) is incorrect.

Step 5 of 5

The dual of resistance is **conductance**. Hence, option (a) is correct.

Thus, the correct answer is option (a).