

Problem

The natural response of an RLC circuit is described by the differential equation

$$\frac{d^2v}{dt^2} + 2 \frac{dv}{dt} + v = 0$$

for which the initial conditions are $v(0) = 10 \text{ V}$ and $dv(0)/dt = 0$. Solve for $v(t)$.

Step-by-step solution

Step 1 of 8

Consider the following differential equation of RLC circuit:

$$\frac{d^2v}{dt^2} + 2 \frac{dv}{dt} + v = 0 \quad \dots\dots (1)$$

Write the generalised expression for RLC circuit.

$$\frac{d^2v}{dt^2} + \frac{R}{L} \frac{dv}{dt} + \frac{1}{LC} v = 0 \quad \dots\dots (2)$$

Here, v is the voltage across the capacitor.

Step 2 of 8

Compare the equations (1) and (2).

$$\frac{R}{L} = 2$$

$$\frac{1}{LC} = 1$$

Calculate the damping factor α .

$$\begin{aligned} \alpha &= \frac{R}{2L} \\ &= \frac{\left(\frac{R}{L}\right)}{2} \end{aligned}$$

Substitute 2 for $\left(\frac{R}{L}\right)$.

$$\begin{aligned} \alpha &= \frac{2}{2} \\ &= 1 \end{aligned}$$

Step 3 of 8

Calculate the undamped natural frequency, ω_0 .

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \sqrt{\frac{1}{LC}}\end{aligned}$$

Substitute 1 for $\frac{1}{LC}$.

$$\begin{aligned}\omega_0 &= \sqrt{1} \\ &= 1\end{aligned}$$

Step 4 of 8

The roots of the characteristic equation are,

$$\begin{aligned}s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ &= -1 \pm \sqrt{1^2 - 1^2} \\ &= -1\end{aligned}$$

The roots of the critically damped system are,

$$\begin{aligned}s_1 &= s_2 \\ &= -\alpha \\ &= -1\end{aligned}$$

Step 5 of 8

Since $\alpha = \omega_0$, the circuit is critically damped and the roots are real and equal. The response of the system is,

$$v(t) = (A_1 + A_2 t)e^{-\alpha t}$$

Substitute 1 for α .

$$v(t) = (A_1 + A_2 t)e^{-t} \dots\dots (3)$$

Substitute 0 for t .

$$\begin{aligned}v(0) &= (A_1 + A_2 \times 0)e^{-0} \\ v(0) &= A_1\end{aligned}$$

Since $v(0) = 10$, substitute 10 for $v(0)$ in above expression.

$$A_1 = 10$$

Step 6 of 8

Recall equation (3).

$$v(t) = (A_1 + A_2 t)e^{-t}$$

Differentiate with respect to t .

$$\begin{aligned}\frac{dv(t)}{dt} &= \frac{d}{dt}(A_1 e^{-t} + A_2 t e^{-t}) \\ &= A_1(-e^{-t}) + A_2(-t e^{-t} + e^{-t})\end{aligned}$$

Substitute 0 for t .

$$\begin{aligned}\frac{dv(0)}{dt} &= A_1(-e^{-0}) + A_2(-0 \times e^{-0} + e^{-0}) \\ &= -A_1 + A_2\end{aligned}$$

Step 7 of 8

Since $\frac{dv(0)}{dt} = 0$, substitute 0 for $\frac{dv(0)}{dt}$ in above expression.

$$0 = -A_1 + A_2$$

$$A_2 = A_1$$

Substitute 10 for A_1 .

$$A_2 = 10$$

Step 8 of 8

Recall equation (3).

$$v(t) = (A_1 + A_2 t)e^{-t}$$

Substitute 10 for A_1 and A_2 .

$$v(t) = (10 + 10t)e^{-t} \text{ V}$$

Therefore, the expression for the voltage, $v(t)$ is $\boxed{(10 + 10t)e^{-t} \text{ V}}$.