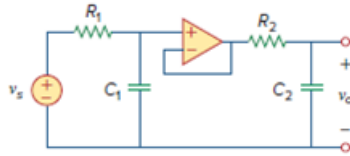


## Problem

In the op amp circuit shown in Fig. 8.34,  $v_s = 25u(t)$  V, find  $v_o(t)$  for  $t > 0$ . Assume that  $R_1 = R_2 = 10\text{ k}\Omega$ ,  $C_1 = 20\text{ }\mu\text{F}$ , and  $C_2 = 100\text{ }\mu\text{F}$ .

Figure 8.34:



## Step-by-step solution

## Step 1 of 14

Refer to Figure 8.34 in the text book for the actual circuit.

At  $t < 0$ , the capacitor acts as open circuit. The value of the voltage source is zero since  $u(t) = 0$  for  $t < 0$ . That is the voltage source acts as short circuit  $t < 0$ .

Draw the circuit diagram at  $t < 0$ .

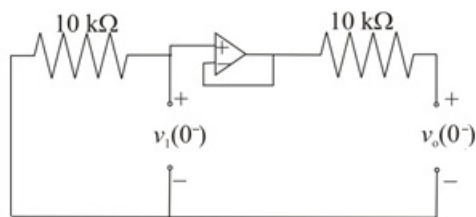


Figure 1

The values of voltages  $v_1(0^-)$  and  $v_o(0^-)$  are  $0\text{ V}$ .

## Step 2 of 14

The value of the voltage source is  $25\text{ V}$  since  $u(t) = 1$  for  $t \geq 0$ .

Draw the circuit diagram at  $t > 0$ .

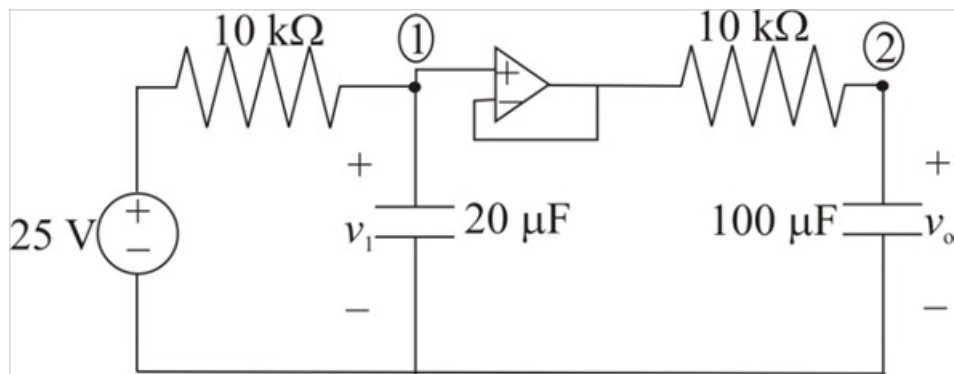


Figure 2

## Step 3 of 14

Buffer amplifier represents same voltage at input and output terminals.

The voltage across the capacitor will not change instantaneously. Hence, at  $t > 0$  the value of the voltages  $v_1(0^+)$  and  $v_o(0^+)$  are  $0\text{ V}$ .

Notice that the voltage across the capacitor is continuous. Therefore, the value of voltages  $v_1(0)$  and  $v_o(0)$  at  $t = 0$  are  $0\text{ V}$ .

#### Step 4 of 14

Apply Kirchhoff's current law at node-1.

$$\frac{v_1 - 25}{10\text{ k}} + (20\text{ }\mu\text{F}) \frac{dv_1}{dt} = 0$$

$$v_1 - 25 + 0.2 \frac{dv_1}{dt} = 0 \dots\dots (1)$$

Calculate the value of  $\frac{dv_1}{dt}$  at  $t = 0$ .

$$0.2 \frac{dv_1(0)}{dt} + v_1(0) - 25 = 0$$

Substitute  $0\text{ V}$  for  $v_1(0)$  and  $v_2(0)$ .

$$0.2 \frac{dv_1(0)}{dt} + (0) - 25 = 0$$

$$0.2 \frac{dv_1(0)}{dt} = 25$$

$$\frac{dv_1(0)}{dt} = 125\text{ V/s}$$

Therefore, the value of the  $\frac{dv_1(0)}{dt}$  is  $125\text{ V/s}$ .

#### Step 5 of 14

Short the voltage source and redraw the circuit to estimate the transient behavior of the circuit.

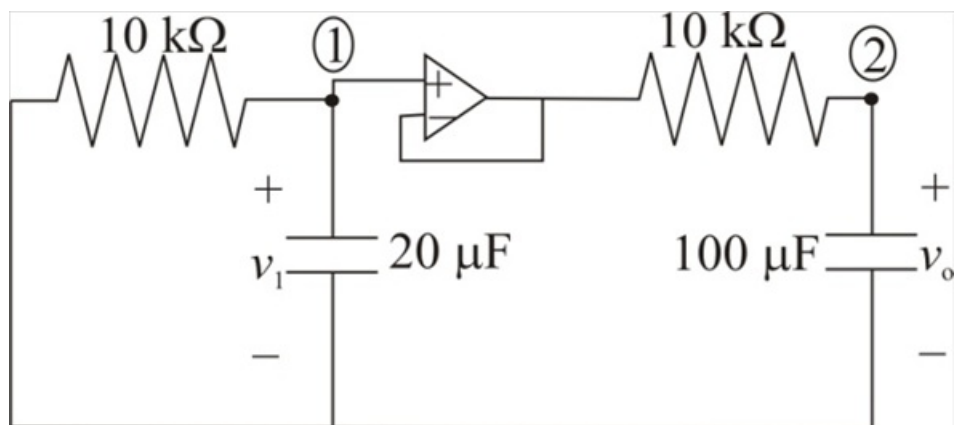


Figure 3

#### Step 6 of 14

Apply Kirchhoff's current law at node-1.

$$\frac{v_1}{10 \text{ k}} + (20 \mu) \frac{dv_1}{dt} = 0$$

$$v_1 + 0.2 \frac{dv_1}{dt} = 0 \dots\dots (2)$$

**Step 7** of 14

Apply Kirchhoff's current law at node-2.

$$(100 \mu) \frac{dv_o}{dt} + \frac{v_o - v_1}{10 \text{ k}} = 0$$

$$\frac{dv_o}{dt} + v_o - v_1 = 0$$

$$v_1 = \frac{dv_o}{dt} + v_o$$

Substitute  $\frac{dv_o}{dt} + v_o$  for  $v_1$  in equation (2).

$$\frac{dv_o}{dt} + v_o + 0.2 \frac{d}{dt} \left( \frac{dv_o}{dt} + v_o \right) = 0$$

$$0.2 \frac{d^2 v_o}{dt^2} + 1.2 \frac{dv_o}{dt} + v_o = 0$$

$$\frac{d^2 v_o}{dt^2} + 6 \frac{dv_o}{dt} + 5 v_o = 0$$

Consider  $\frac{di}{dt}$  as  $s$ .

$$s^2 v_o + 6s v_o + 5 v_o = 0$$

$$(s^2 + 6s + 5) v_o = 0$$

**Step 8** of 14

Consider the characteristic equation of the transient circuit.

$$s^2 + 6s + 5 = 0$$

$$(s + 1)(s + 5) = 0$$

The roots of the characteristic equation are  $s_1 = -1$  and  $s_2 = -5$ .

**Step 9** of 14

Consider the expression for the voltage  $v_{0t}$  in transient state.

$$v_{0t} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Substitute  $-1$  for  $s_1$  and  $-5$  for  $s_2$ .

$$v_{0t} = A_1 e^{-t} + A_2 e^{-5t}$$

**Step 10** of 14

At  $t = \infty$ , as steady state is reached, capacitors are open circuited.

Draw the circuit diagram at  $t = \infty$ .

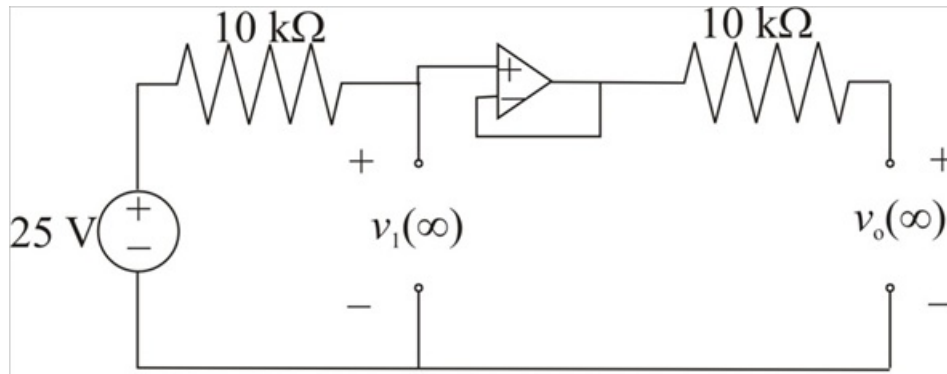


Figure 4

The values of voltages  $v_1(\infty)$  and  $v_2(\infty)$  are 25 V.

#### Step 11 of 14

Notice that the roots are negative and real, hence the circuit exhibits over damped response.

Consider the expression for the voltage  $v_1(t)$  for complete response.

$$v_0(t) = v_{0t}(t) + v_{0ss}(t)$$

Here  $v_{0t}(t)$  represents the transient response,

$v_{0ss}(t)$  represents the steady state response that is  $v_1(\infty)$

$$v_0(t) = v_0 + v_0(\infty)$$

Substitute 25 V for  $v_0(\infty)$  and  $A_1 e^{-t} + A_2 e^{-5t}$  for  $v_{0t}$ .

$$v_0(t) = A_1 e^{-t} + A_2 e^{-5t} + 25 \dots\dots (3)$$

#### Step 12 of 14

Recall equation (3).

$$v_0(t) = A_1 e^{-t} + A_2 e^{-5t} + 25$$

Substitute 0 for  $t$ .

$$v_0(0) = A_1 e^{-(0)} + A_2 e^{-5(0)} + 25$$

Substitute 0 V for  $v_0(0)$ .

$$0 = A_1 e^{(0)} + A_2 e^{(0)} + 25$$

$$0 = A_1(1) + A_2(1) + 25$$

$$0 = A_1 + A_2 + 25$$

$$A_1 = -A_2 - 25 \dots\dots (4)$$

Recall equation (3).

$$v_0(t) = A_1 e^{-t} + A_2 e^{-5t} + 25$$

Apply derivative with respect to  $t$ .

$$\begin{aligned} \frac{dv_0(t)}{dt} &= A_1 \frac{d(e^{-t})}{dt} + A_2 \frac{d(e^{-5t})}{dt} + \frac{d(25)}{dt} \\ &= -A_1 e^{-t} - 5A_2 e^{-5t} + 0 \\ &= -A_1 e^{-t} - 5A_2 e^{-5t} \end{aligned}$$

Substitute 0 for  $t$ .

$$\begin{aligned} \frac{dv_0(0)}{dt} &= -A_1 e^{(0)} - 5A_2 e^{(0)} \\ &= -A_1(1) - 5A_2(1) \\ &= -A_1 - 5A_2 \end{aligned}$$

Substitute 0 for  $\frac{dv_0(0)}{dt}$  and  $-A_2 - 25$  for  $A_1$ .

$$0 = -(-A_2 - 25) - 5A_2$$

$$0 = A_2 + 25 - 5A_2$$

$$0 - 25 = -4A_2$$

$$\begin{aligned} A_2 &= \frac{25}{4} \\ &= 6.25 \end{aligned}$$

Therefore, the value of the constant  $A_2$  is 6.25.

#### Step 13 of 14

Recall equation (3).

$$A_1 = -A_2 - 25$$

Substitute 6.25 for  $A_2$ .

$$\begin{aligned} A_1 &= -(6.25) - 25 \\ &= -31.25 \end{aligned}$$

Therefore, the value of the constant  $A_1$  is, -31.25.

#### Step 14 of 14

Recall equation (3).

$$v_0(t) = A_1 e^{-t} + A_2 e^{-5t} + 25$$

Substitute 6.25 for  $A_2$  and  $-31.25$  for  $A_1$ .

$$v_0(t) = 25 - 31.25e^{-t} + 6.25e^{-5t}$$

Therefore, the value of the voltage  $v_0(t)$  is  $25 - 31.25e^{-t} + 6.25e^{-5t}$ .

Therefore, the value of the voltage  $v_0$  is  $\boxed{25 - 31.25e^{-t} + 6.25e^{-5t} \text{ V}, t > 0}$ .