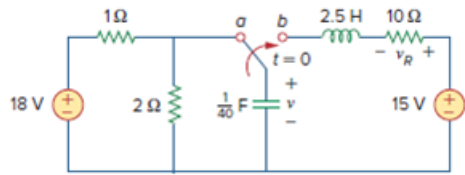


## Problem

Refer to the circuit in Fig. 8.21 (see Practice Prob. 8.7). Use *PSpice* to obtain  $v(t)$  for  $0 < t < 2$ .

**Fig. 8.21:**



## Step-by-step solution

## Step 1 of 11

Refer to Figure 8.21 in the textbook.

Draw the modified circuit for  $t < 0$ .

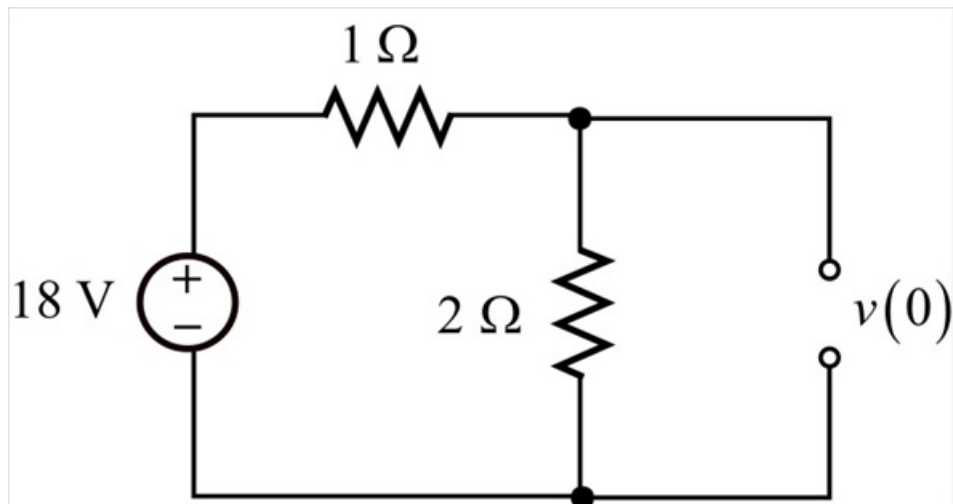


Figure 1

## Step 2 of 11

Apply voltage division rule to calculate the initial voltage,  $v(0)$ .

$$\begin{aligned} v(0) &= \left[ \frac{2}{2+1} \right] (18) \\ &= \left[ \frac{2}{3} \right] (18) \\ &= 12 \text{ V} \end{aligned}$$

The inductor current is independent of the circuit.

$$i(0) = 0 \text{ A}$$

## Step 3 of 11

Draw the modified circuit for  $t > 0$ .

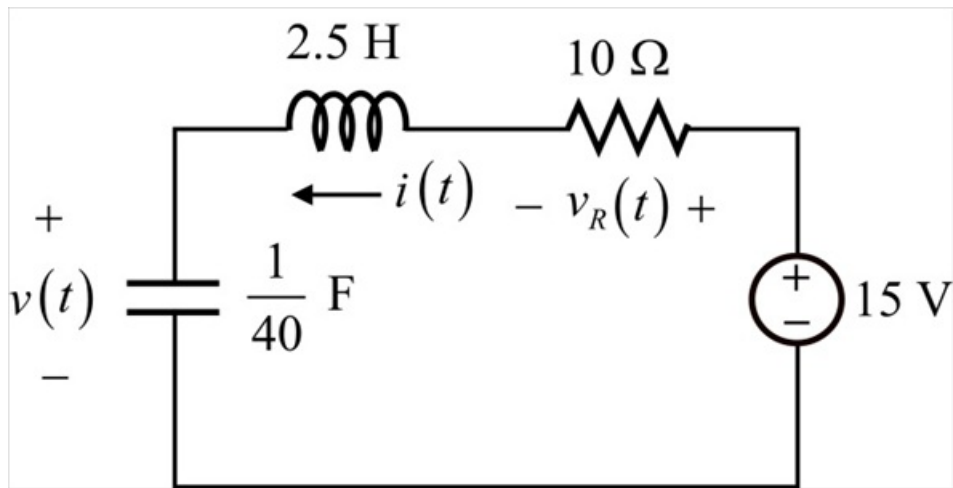


Figure 2

**Step 4** of 11

Calculate the value of  $\alpha$ .

$$\alpha = \frac{R}{2L}$$

Substitute  $10 \Omega$  for  $R$  and  $2.5 \text{ H}$  for  $L$ .

$$\begin{aligned}\alpha &= \frac{10}{2(2.5)} \\ &= \frac{10}{5} \\ &= 2\end{aligned}$$

Calculate the value of  $\omega_0$ .

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Substitute  $\frac{1}{40} \text{ F}$  for  $C$  and  $2.5 \text{ H}$  for  $L$ .

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{2.5 \cdot \frac{1}{40}}} \\ &= \sqrt{16} \\ &= 4\end{aligned}$$

**Step 5** of 11

Since  $\omega_0 > \alpha$ , the response is under damped.

Calculate the characteristics of the system.

$$\begin{aligned}s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \\ &= -2 \pm \sqrt{4 - 16} \\ &= -2 \pm j3.464\end{aligned}$$

Calculate the total response.

$$v(t) = v_{ss} + (A_1 \cos \omega_d t + A_2 \sin \omega_d t) e^{-2t}$$

Here,  $v_{ss}$  is the steady state response. It is the final value of the capacitor voltage.

From the circuit, as  $t \rightarrow \infty$ , circuit reaches steady state and capacitor is replaced with open circuit and inductor with short circuit.

Draw the modified circuit with for  $t \rightarrow \infty$ .

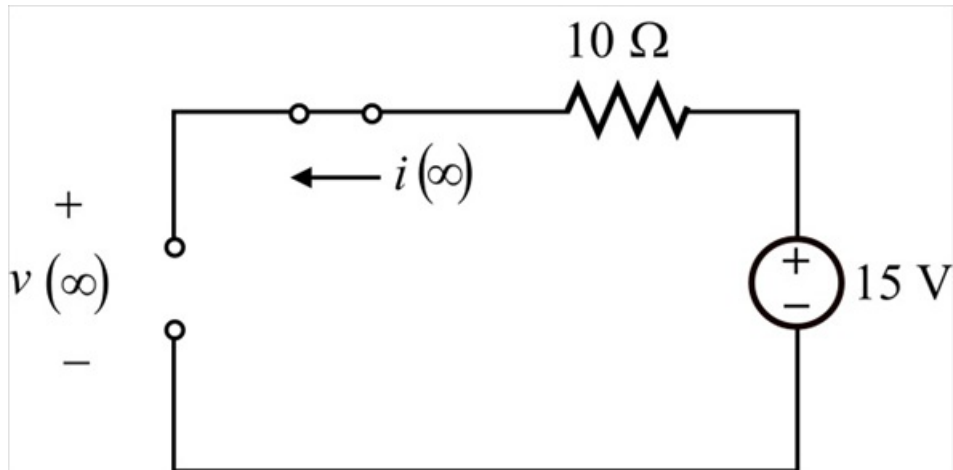


Figure 3

### Step 7 of 11

The steady state value is,

$$\begin{aligned} v_{ss} &= v(\infty) \\ &= 15 \text{ V} \end{aligned}$$

Substitute 15 V for  $v_{ss}$  in  $v(t)$ .

$$v(t) = 15 + (A_1 \cos 3.464t + A_2 \sin 3.464t) e^{-2t}$$

Substitute 0 for  $t$ .

$$\begin{aligned} v(0) &= 15 + (A_1 \cos 3.464(0) + A_2 \sin 3.464(0)) \\ 12 &= 15 + A_1 \\ A_1 &= -3 \end{aligned}$$

### Step 8 of 11

At  $t = 0^+$ , the inductor and capacitor are in series, so the current passing through it is same.

$$\begin{aligned} i(0) &= C \frac{dv(0)}{dt} \\ \frac{dv(0)}{dt} &= \frac{i(0)}{C} \\ \frac{dv(0)}{dt} &= \frac{0}{\left(\frac{1}{40}\right)} \\ \frac{dv(0)}{dt} &= 0 \text{ V/s} \end{aligned}$$

Differentiate the function  $v(t)$  with respect to  $t$ .

$$\begin{aligned} \frac{dv(t)}{dt} &= \frac{d}{dt} [15 + (A_1 \cos 3.464t + A_2 \sin 3.464t) e^{-2t}] \\ &= \begin{bmatrix} -2e^{-2t} (A_1 \cos 3.464t + A_2 \sin 3.464t) \\ + e^{-2t} (-3.464 A_1 \sin 3.464t + 3.464 A_2 \cos 3.464t) \end{bmatrix} \end{aligned}$$

Substitute 0 for  $t$ .

$$\frac{dv(0)}{dt} = -2A_1 + 3.464A_2$$

Substitute 0 for  $\frac{dv(0)}{dt}$  and  $-3$  for  $A_1$ .

$$0 = -2(-3) + 3.464A_2$$

$$3.464A_2 = -6$$

$$A_2 = -1.7321$$

Substitute  $-1.7321$  for  $A_2$  and  $-3$  for  $A_1$  in  $v(t)$ .

$$\begin{aligned} v(t) &= 15 + e^{-2t}[-3\cos(3.464t) - 1.7321\sin(3.464t)] \text{ V} \\ &= 15 - e^{-2t}[3\cos(3.464t) + 1.7321\sin(3.464t)] \text{ V} \end{aligned}$$

Hence, the voltage across the capacitor is,

$$15 - e^{-2t}[3\cos(3.464t) + 1.7321\sin(3.464t)] \text{ V}$$

## Step 10 of 11

Draw the circuit in Pspice.

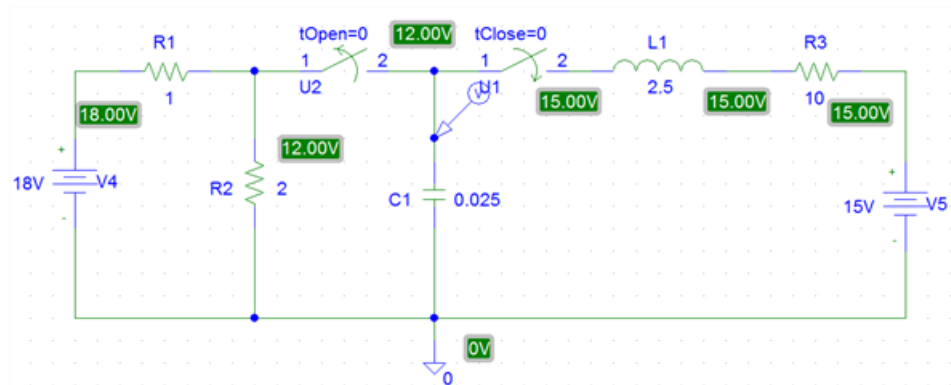


Figure 4

## Step 11 of 11

Draw the following output:

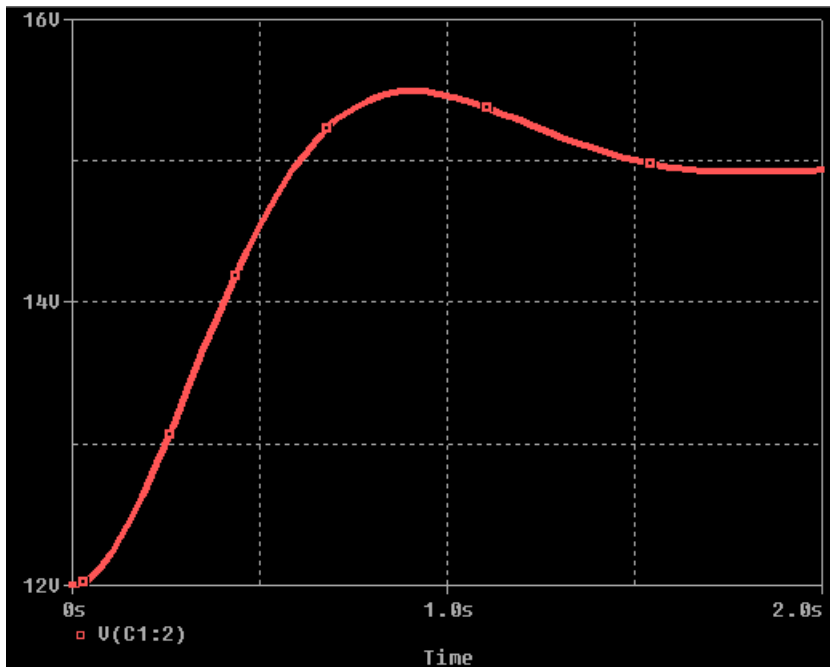


Figure 5