

Problem

The responses of a series RLC circuit are

$$v_C(t) = 30 - 10e^{-20t} + 30e^{-10t} \text{ V}$$

$$i_L(t) = 40e^{-20t} - 60e^{-10t} \text{ mA}$$

where v_C and i_L are the capacitor voltage and inductor current, respectively. Determine the values of R , L , and C .

Step-by-step solution

Step 1 of 3

We have series RLC circuit

$$V_L(t) = 30 - 10e^{-20t} + 30e^{-30t}$$

$$\Leftrightarrow V(t) = V_s + A_1 e^{s_1 t} + A_2 e^{s_2 t} \quad [\alpha > \omega_0]$$

$$i_L(t) = 40e^{-20t} - 60e^{-10t} \text{ mA}$$

$$\Leftrightarrow i(t) = A_1' e^{s_1 t} + A_2' e^{s_2 t} \quad [\alpha > \omega_0]$$

Comparing these equations, we get

$$V_s = 30$$

$$A_1 = -10 ; A_2 = 30 ;$$

$$S_1 = -20 ; S_2 = -10 \rightarrow (1)$$

$$A_1' = 40 ; A_2' = -60 ;$$

$$S_1' = -20 ; S_2' = -10 \rightarrow (2)$$

Step 2 of 3

Now, From equation (1) and equation(2),

$$S_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad \text{And} \quad S_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$S_1 + S_2 = -2\alpha \quad \text{And} \quad S_1 S_2 = \omega_0^2$$

$$\left[\text{Where } \alpha = \frac{R}{2L} ; \omega_0 = \frac{1}{\sqrt{LC}} \right]$$

$$\Rightarrow -30 = -2\alpha$$

$$\Rightarrow \alpha = 15$$

$$\Rightarrow \frac{R}{2L} = 15 \rightarrow (3)$$

$$200 = \omega_0^2 \Rightarrow \frac{1}{LC} = 200 \rightarrow (4)$$

Step 3 of 3

$$\text{Also, } i(t) = C \frac{dV(t)}{dt} = C[200e^{-20t} - 300e^{-10t}]$$

$$\text{Or, } (A_1' e^{S_1 t} + A_2' e^{S_2 t}) \times 10^{-3} A = C \{ [200e^{-20t} - 300e^{-10t}] V \}$$

$$[S_1 = S_1', S_2 = S_2']$$

$$\Rightarrow 200C = A_1' = 40 \times 10^{-3}$$

$$\Rightarrow C = 200 \times 10^{-6} F \Rightarrow C = 200 \mu F$$

And hence, by using equations (3) and (4) we get,

$$L = \frac{1}{200C} F = \frac{1}{200 \times 200 \times 10^{-6}} = 25 H$$

$$\text{And, } R = 30L = 30 \times 25 = 750 \Omega$$