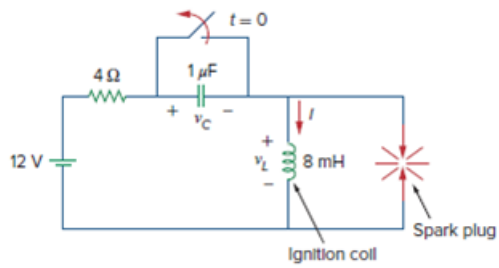


Problem

In Fig. 8.52, find the capacitor voltage v_C for $t > 0$.


Figure 8.52:



Step-by-step solution

Step 1 of 13


The given circuit is,

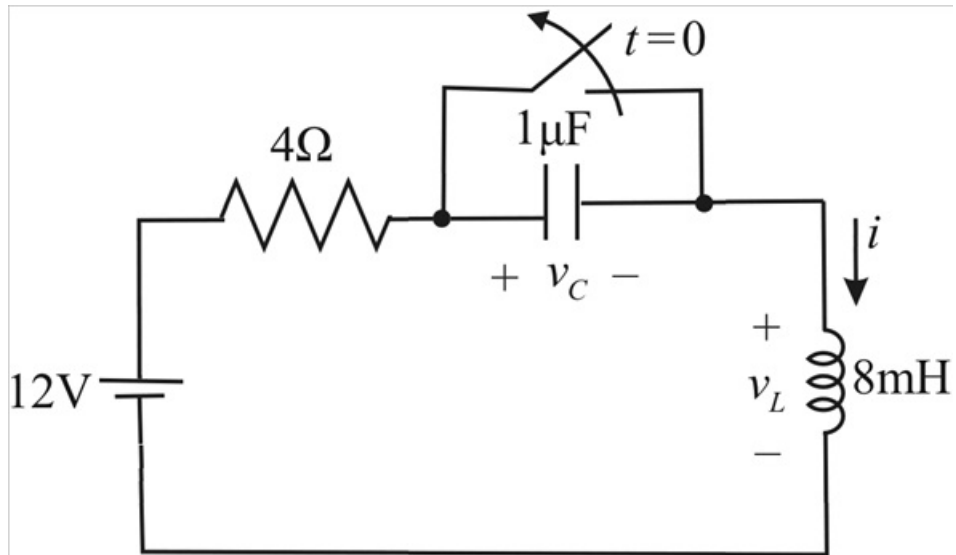

Step 2 of 13

The switch is closed for $t < 0$ and the circuit is in steady state, therefore the capacitor is replaced with an open circuit and the inductor is replaced with a short circuit as shown,

Step 3 of 13

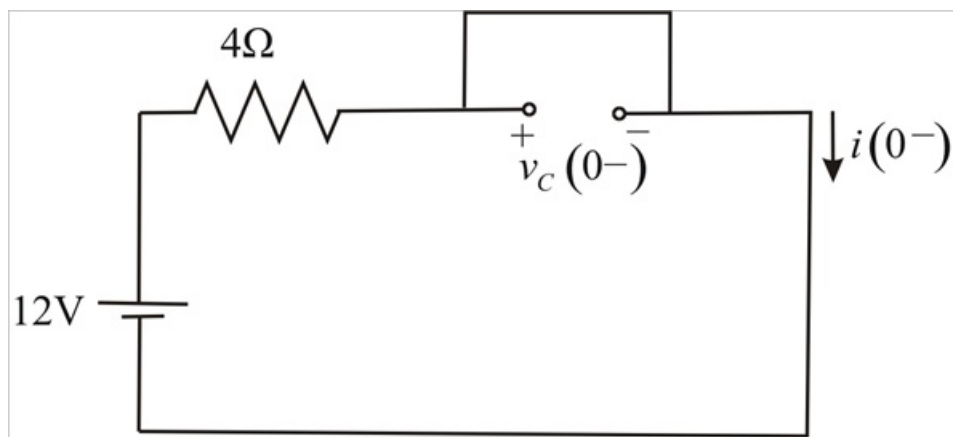

Step 4 of 13

$$v_C(0^-) = 0V$$

$$i(0^-) = \frac{12}{4}$$

$$i(0^-) = 3A$$

Due to the continuity of the capacitor voltage and inductor current,

$$v_C(0^+) = v_C(0^-)$$


$$v_C(0^+) = 0V$$

$$i(0^+) = i(0^-)$$

$$i(0^+) = 3A$$

Step 5 of 13

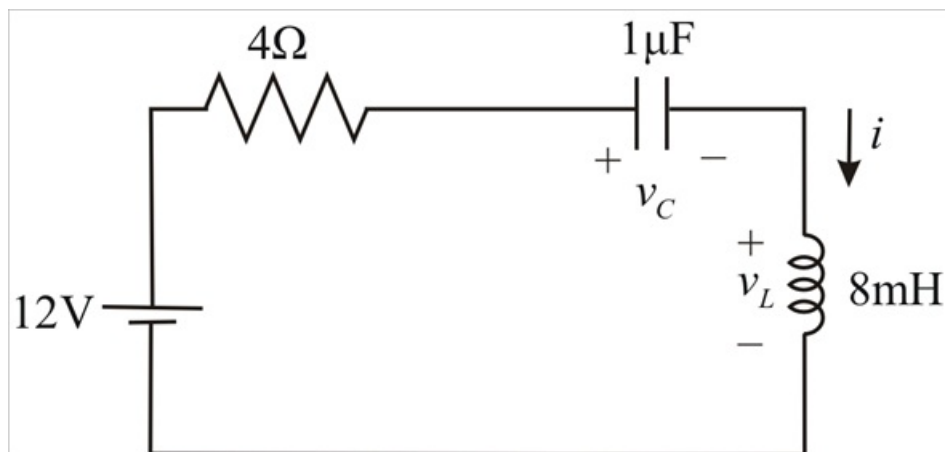For $t > 0$, the switch opened, therefore the equivalent circuit is,



Step 6 of 13

The current through the capacitor at $t=0^+$ is

$$i(0^+) = C \frac{dv_C(0^+)}{dt}$$

$$\frac{dv_C(0^+)}{dt} = \frac{i(0^+)}{C}$$

$$\frac{dv_C(0^+)}{dt} = \frac{3}{1\mu}$$

$$\frac{dv_C(0^+)}{dt} = 3 \times 10^6 \text{ V/s}$$

Step 7 of 13

The circuit is a series RLC circuit,

$$\alpha = \frac{R}{2L}$$

$$\alpha = \frac{4}{2(8 \times 10^{-3})}$$

$$\alpha = 250$$

$$\alpha^2 = 62500$$

Step 8 of 13

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\omega_0 = \frac{1}{\sqrt{(8 \times 10^{-3})(1 \times 10^{-6})}}$$

$$\omega_0^2 = 125 \times 10^6$$

Since $\omega_0^2 > \alpha^2$, the response is under damped therefore the form of the transient response is

$$v_{Cr}(t) = e^{-250t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

$$\omega_d = 11180$$

Therefore

$$v_{Cr}(t) = e^{-250t} (B_1 \cos 11180t + B_2 \sin 11180t)$$


Step 9 of 13

The steady state response is,

$$v_{C_{ss}}(t) = v_C(\infty)$$

As $t \rightarrow \infty$, the circuit reaches steady state condition and the capacitor is replaced by an open circuit and the inductor is replaced by a short circuit,

Step 10 of 13

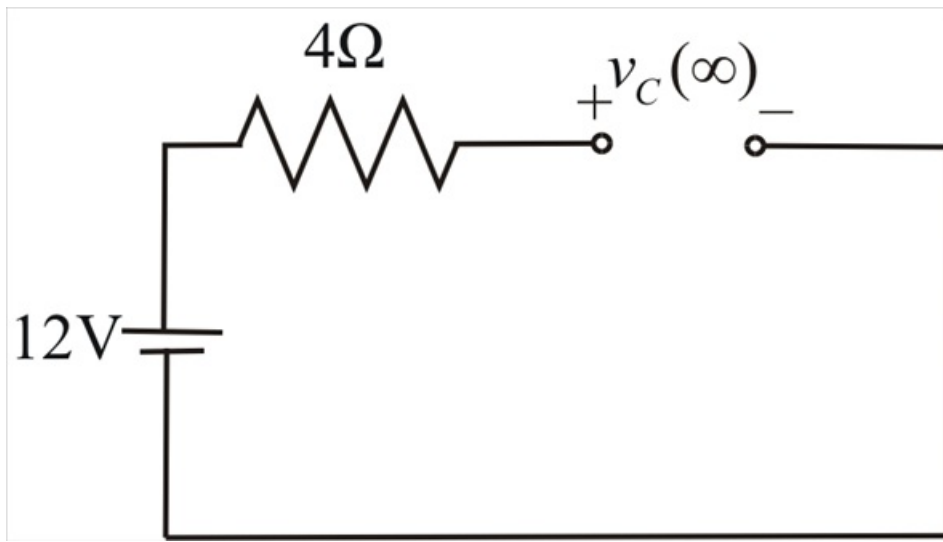

Step 11 of 13

From above circuit,

$$v_C(\infty) = 12\text{V}$$

Hence $v_{C_{ss}}(t) = 12\text{V}$

Therefore, the complete response,

$$v_C(t) = v_{C_r}(t) + v_{C_{ss}}(t)$$

$$v_C(t) = 12 + e^{-250t} (B_1 \cos 11180t + B_2 \sin 11180t) \dots\dots\dots (1)$$

Step 12 of 13

Using initial conditions, at $t=0$

$$v_C(0) = 12 + B_1$$

$$0 = 12 + B_1$$

$$B_1 = -12$$

Taking the derivative of $v_C(t)$ in equation (1), we get

$$\begin{aligned} \frac{dv_C(t)}{dt} = & -250e^{-250t} (B_1 \cos 11180t + B_2 \sin 11180t) \\ & + e^{-250t} (-11180B_1 \sin 11180t + 11180B_2 \cos 11180t) \end{aligned}$$

Step 13 of 13

At $t=0^+$

$$\frac{dv_c(0^+)}{dt} = -250 B_1 + 11180 B_2$$

$$3 \times 10^6 = -250(-12) + 11180 B_2$$

$$11180 B_2 = 3 \times 10^6 - 3000$$

$$B_2 = 268.07$$

The total response is,

$$\therefore v_c(t) = (12 - 12e^{-250t} \cos 11180t + 268.07e^{-250t} \sin 11180t) \text{ V}$$