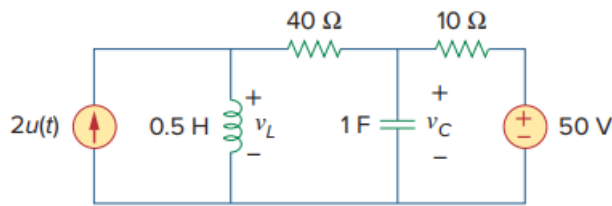


Problem

Consider the circuit in Fig. 8.79. Find $v_L(0^+)$ and $v_C(0^+)$.

Figure 8.79:



Step-by-step solution

Step 1 of 6

Refer to figure 8.79 in the textbook.

Define the input current.

$$2u(t) = \begin{cases} 0 \text{ A}, & t < 0 \\ 2 \text{ A}, & t > 0 \end{cases}$$

Redraw the circuit for $t < 0$ as shown in figure 1.

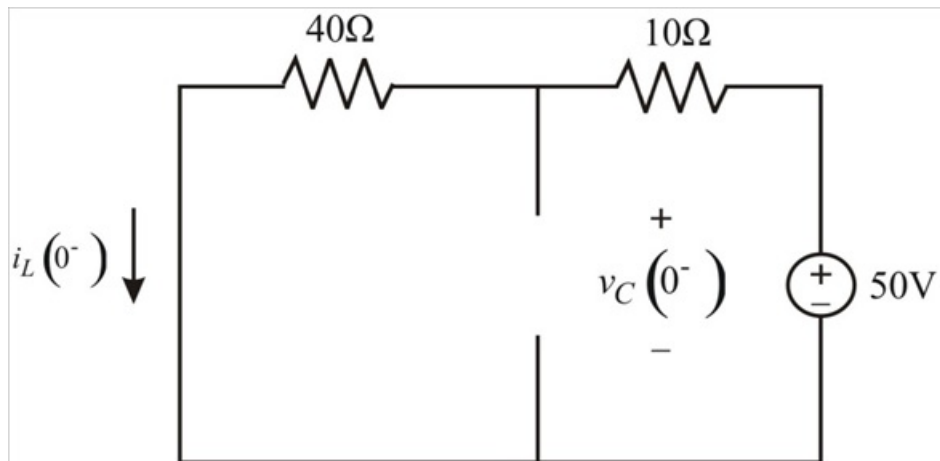


Figure 1

Step 2 of 6

Calculate the initial voltage across the capacitor.

Apply the voltage division rule to the circuit shown in figure 1.

$$v_C(0^-) = \frac{40}{40 + 10} \times 50 \\ = 40 \text{ V}$$

The capacitor doesn't allow sudden changes in voltage.

$$v_C(0^-) = v_C(0^+) = 40 \text{ V}$$

Therefore, the voltage $v_C(0^+)$ is 40 V.

Step 3 of 6

Calculate the initial current through the inductor.

Apply Ohm's law to the circuit shown in figure 1.


$$\begin{aligned} i_L(0^-) &= \frac{50}{40+10} \\ &= \frac{50}{50} \\ &= 1 \text{ A} \end{aligned}$$

The inductor doesn't allow sudden changes in current.

$$i_L(0^-) = i_L(0^+) = 1 \text{ A}$$

Step 4 of 6

Draw the circuit for $t = 0^+$ as shown in figure 2.

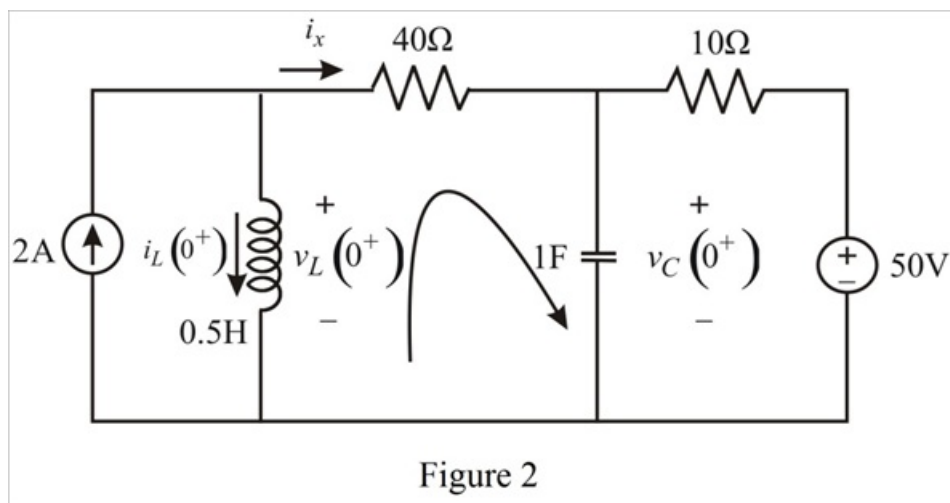**Step 5** of 6

Apply Kirchhoff's current law at the input node of the circuit shown in figure 2.

$$i_x + i_L(0^+) = 2$$

$$i_x = 2 - i_L(0^+)$$

Substitute 1 for $i_L(0^+)$.

$$\begin{aligned} i_x &= 2 - 1 \\ &= 1 \text{ A} \end{aligned}$$

Step 6 of 6

Apply Kirchhoff's voltage law around the centre loop of the circuit shown in figure 2.

$$-v_L(0^+) + 40i_x + v_C(0^+) = 0$$

$$v_L(0^+) = 40i_x + v_C(0^+)$$

Substitute 1 for i_x , and 40 for $v_C(0^+)$.

$$\begin{aligned} v_L(0^+) &= 40 \times 1 + 40 \\ &= 80 \text{ V} \end{aligned}$$

Therefore, the value of $v_L(0^+)$ is 80 V.