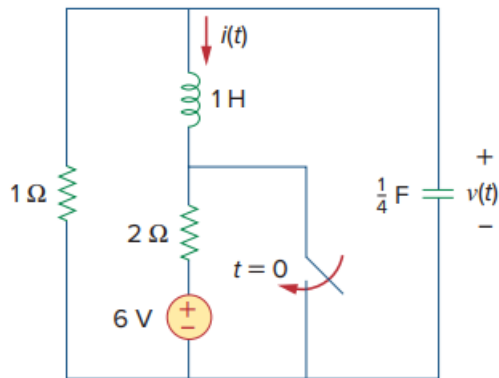


Problem

Given the circuit in Fig. 8.95, find $i(t)$ and $v(t)$ for $t > 0$.

Figure 8.95:



Step-by-step solution

Step 1 of 11

The following is the given circuit diagram:

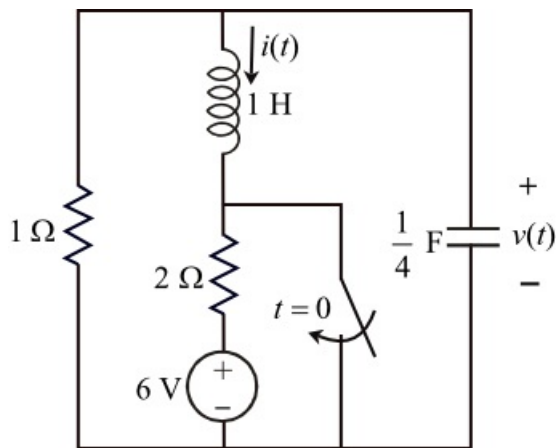


Figure 1

Step 2 of 11

For $t < 0$, the switch is in open position and the circuit is in steady state, therefore the capacitor is replaced by an open circuit and the inductor by a short circuit as shown in Figure 2.

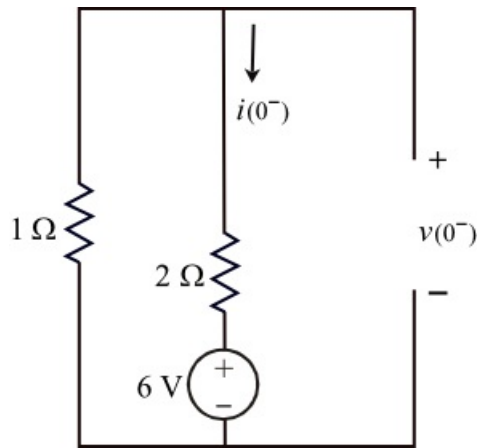


Figure 2

Step 3 of 11

Apply Kirchhoff's voltage law to the left side loop of Figure 2.

$$2i(0^-) + 6 + 1i(0^-) = 0$$

$$i(0^-) = \frac{-6}{2+1}$$

$$i(0^-) = -2 \text{ A}$$

Apply Kirchhoff's voltage law to the right side loop of Figure 2.

$$2i(0^-) + 6 - v(0^-) = 0$$

$$\begin{aligned} v(0^-) &= 2i(0^-) + 6 \\ &= 2(-2) + 6 \\ &= 2 \text{ V} \end{aligned}$$

Step 4 of 11

Since the capacitor voltage and inductor current cannot change instantaneously.

$$v(0^-) = v(0) = 2 \text{ V}$$

$$i(0^-) = i(0) = -2 \text{ A}$$

Step 5 of 11

For $t > 0$, the switch is closed, we remove the voltage source and the $2\ \Omega$ resistor as they are in parallel with a short circuit. Therefore the equivalent circuit is shown in Figure 3.

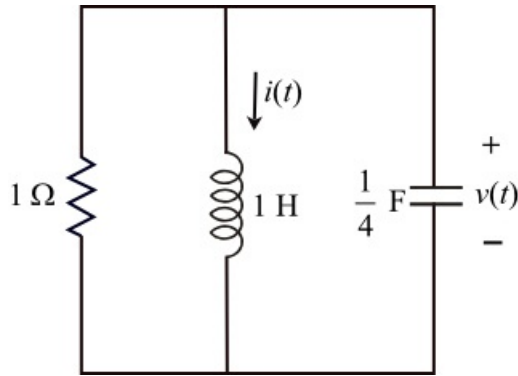


Figure 3

Step 6 of 11

It is a parallel RLC circuit. Therefore, the neper frequency is,

$$\begin{aligned}\alpha &= \frac{1}{2RC} \\ &= \frac{1}{2(1)\left(\frac{1}{4}\right)} \\ &= 2 \text{ rad/s}\end{aligned}$$

The resonant frequency is,

$$\begin{aligned}\omega_o &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{(1)\left(\frac{1}{4}\right)}} \\ &= 2 \text{ rad/s}\end{aligned}$$

Step 7 of 11

Since $\alpha = \omega_o$, the response is critically damped and the roots are,

$$\begin{aligned}s_{1,2} &= -\alpha \pm \sqrt{\alpha^2 - \omega_o^2} \\ &= -2 \pm \sqrt{2^2 - 2^2} \\ &= -2\end{aligned}$$

Therefore, the voltage across the capacitor is,

$$\begin{aligned}v(t) &= (A_1 + A_2 t)e^{-\alpha t} \\ v(t) &= (A_1 + A_2 t)e^{-2t} \dots\dots (1)\end{aligned}$$

Applying initial conditions, at $t = 0$

$$\begin{aligned}v(0) &= (A_1 + A_2(0))e^{-2(0)} \\ &= A_1\end{aligned}$$

Substitute $v(0)$ in the above equation.

Therefore, $A_1 = 2$

Step 8 of 11

Differentiate the equation (1) with respect to t.

$$\frac{dv(t)}{dt} = -2e^{-2t}(A_1 + A_2t) + e^{-2t}A_2$$

At $t = 0^+$,

$$\begin{aligned}\frac{dv(0^+)}{dt} &= -2e^{-2(0)}(A_1 + A_2(0)) + e^{-2(0)}A_2 \\ &= -2A_1 + A_2 \\ &= -2(2) + A_2\end{aligned}$$

$$\frac{dv(0^+)}{dt} = -4 + A_2 \dots\dots (2)$$

Step 9 of 11

Apply Kirchhoff's current law at top node of Figure 3.

$$\frac{v(t)}{1} + i(t) + \frac{1}{4} \frac{dv(t)}{dt} = 0 \dots\dots (3)$$

At $t = 0^+$,

$$\begin{aligned}\frac{v(0)}{1} + i(0) + \frac{1}{4} \frac{dv(0)}{dt} &= 0 \\ 2 + (-2) + \frac{1}{4} \frac{dv(0)}{dt} &= 0 \\ \frac{1}{4} \frac{dv(0)}{dt} &= 0 \\ \frac{dv(0)}{dt} &= 0\end{aligned}$$

Step 10 of 11

Substitute $\frac{dv(0)}{dt} = 0$ in equation (2).

$$\begin{aligned}0 &= -4 + A_2 \\ A_2 &= 4\end{aligned}$$

Substitute $A_1 = 2$ and $A_2 = 4$ in equation (1).

$$\begin{aligned}v(t) &= (2 + 4t)e^{-2t} \\ &= 2(1 + 2t)e^{-2t} \text{ V}\end{aligned}$$

Therefore, the voltage across the capacitor, $v(t)$ for $t > 0$ is $\boxed{2(1 + 2t)e^{-2t} \text{ V}}$.

Step 11 of 11

From equation (3), the current through inductor is,

$$\begin{aligned} i(t) &= -\left(v(t) + \frac{1}{4} \frac{dv(t)}{dt} \right) \\ &= -\left((2+4t)e^{-2t} + \frac{1}{4} \frac{d((2+4t)e^{-2t})}{dt} \right) \\ &= -\left((2+4t)e^{-2t} + \frac{1}{4} [(-2)(2)e^{-2t} + 4(e^{-2t} + t(-2)e^{-2t})] \right) \\ &= -\left((2+4t)e^{-2t} + \frac{1}{4} [-4e^{-2t} + (4e^{-2t} - 8te^{-2t})] \right) \\ &= -\left((2+4t)e^{-2t} + \frac{1}{4} [-8te^{-2t}] \right) \\ &= -(2+4t)e^{-2t} - 2te^{-2t} \\ &= (-2-2t)e^{-2t} \text{ A} \end{aligned}$$

Therefore, the current through the inductor, $i(t)$ for $t > 0$ is $\boxed{(-2-2t)e^{-2t} \text{ A}}$.