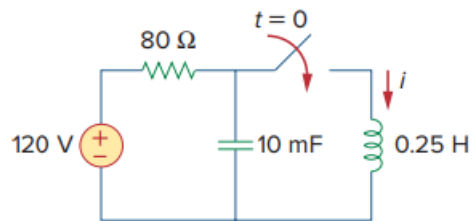


Problem

After being open for a day, the switch in the circuit of Fig. 8.99 is closed at $t = 0$. Find the differential equation describing $i(t)$, $t > 0$.

Figure 8.99:



Step-by-step solution

Step 1 of 3

Refer to circuit diagram in Figure 8.99 in the textbook.

At $t > 0$ the switch in the circuit is closed. The circuit diagram at $t > 0$ is shown in Figure 1.

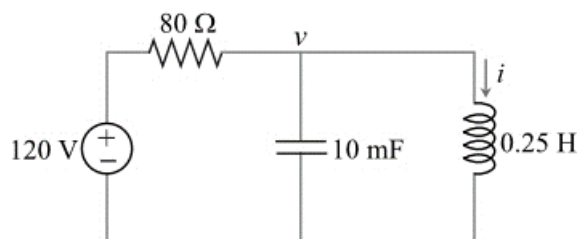


Figure 1

Step 2 of 3

The voltage across the inductor is,

$$\begin{aligned} v_L &= L \frac{di}{dt} \\ &= 0.25 \frac{di}{dt} \end{aligned}$$

In the circuit shown in Figure 1, capacitor and inductor are connected in parallel.

It is known that, in parallel connection the voltage across each element is same. Therefore,

$$\begin{aligned} v &= v_L \\ &= 0.25 \frac{di}{dt} \end{aligned}$$

Step 3 of 3

Apply the Kirchhoff's current law at node v .

$$\frac{v-120}{80} + (10 \times 10^{-3}) \frac{dv}{dt} + i = 0$$

Substitute $0.25 \left(\frac{di}{dt} \right)$ for v .

$$\frac{0.25 \frac{di}{dt} - 120}{80} + (10 \times 10^{-3}) \frac{d}{dt} \left(0.25 \frac{di}{dt} \right) + i = 0$$

$$0.25 \frac{di}{dt} - 120 + (80)(0.25)(10 \times 10^{-3}) \frac{d^2 i}{dt^2} + 80i = 0$$

$$0.2 \frac{d^2 i}{dt^2} + 0.25 \frac{di}{dt} - 120 + 80i = 0$$

$$\frac{d^2 i}{dt^2} + \frac{0.25}{0.2} \frac{di}{dt} + \frac{80}{0.2} i = \frac{120}{0.2}$$

$$\frac{d^2 i}{dt^2} + 1.25 \frac{di}{dt} + 400i = 600$$

Therefore, the differential equation for $i(t)$ is $\boxed{\frac{d^2 i}{dt^2} + 1.25 \frac{di}{dt} + 400i = 600}$.