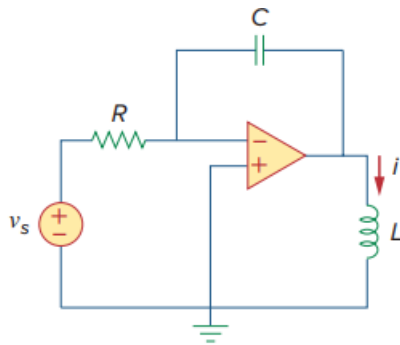


Problem

For the op amp circuit in Fig. 8.108, find the differential equation for $i(t)$.

Figure 8.108:



Step-by-step solution

Step 1 of 3

Consider the following circuit diagram.

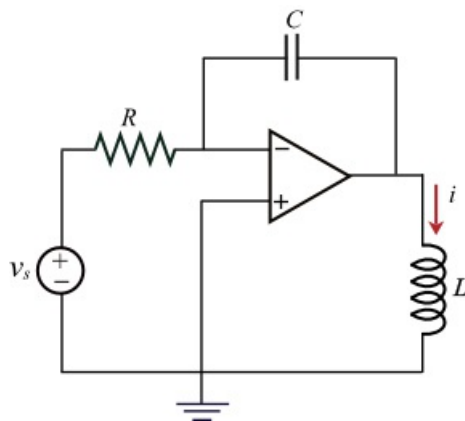


Figure 1

Step 2 of 3

The voltage at the inverting and the non-inverting terminals are equal and it is equal to zero in Figure 1 by the virtual ground concept.

Redraw the circuit in Figure 1 after indicating the voltages at the nodes.

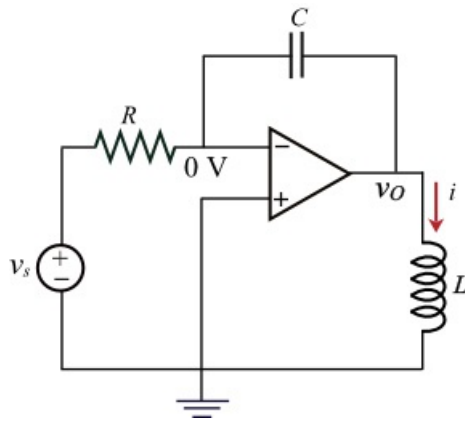


Figure 2

Step 3 of 3

Apply the Kirchhoff's current law at the inverting terminal of the op-amp.

$$\frac{0 - v_s}{R} + i_c = 0$$

$$\frac{0 - v_s}{R} + C \left[\frac{d}{dt} (0 - v_o) \right] = 0$$

Substitute the expression $L \frac{di}{dt}$ for output voltage v_o .

$$\frac{-v_s}{R} + C \left[\frac{d}{dt} \left(-L \frac{di}{dt} \right) \right] = 0$$

$$\frac{-v_s}{R} - LC \left(\frac{d^2 i}{dt^2} \right) = 0$$

$$\frac{d^2 i}{dt^2} = \frac{-v_s}{RLC}$$

Thus, the differential equation for $i(t)$ which is second order is $\frac{-v_s}{RLC}$.