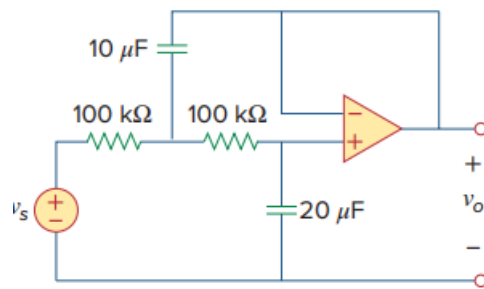


Problem

Obtain the differential equations for $v_o(t)$ in the op amp circuit of Fig. 8.111.

Figure 8.111:



Step-by-step solution

Step 1 of 3

Refer to the Figure 8.66 in the textbook,.

The circuit is a voltage follower therefore, the voltage across the capacitor $20\text{ }\mu\text{F}$ is v_o . The circuit diagram with current directions at node 1 and 2 is shown in Figure 1.

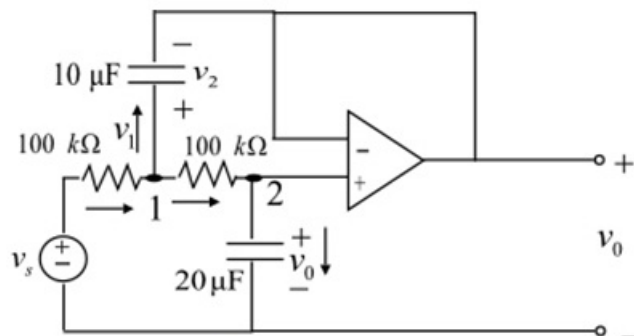


Figure 1

Step 2 of 3

Apply the Kirchhoff's current law at node 1.

$$\frac{v_s - v_1}{100 \times 10^3} = 10 \times 10^{-6} \frac{dv_2}{dt} + \frac{v_1 - v_0}{100 \times 10^3} \dots\dots (1)$$

Apply the Kirchhoff's current law at node 2.

$$\frac{v_1 - v_0}{100 \times 10^3} = (20 \times 10^{-6}) \frac{dv_0}{dt} \dots\dots (2)$$

Due to virtual ground, there will be no current flow in the operational amplifier.

Therefore,

$$v_2 = v_1 - v_0$$

Eliminate the values of v_2 and $\frac{v_1 - v_0}{100 \times 10^3}$ in equation (1).

$$\frac{v_s - v_1}{100 \times 10^3} = 10 \times 10^{-6} \frac{dv_1}{dt} - 10 \times 10^{-6} \frac{dv_0}{dt} + (20 \times 10^{-6}) \frac{dv_0}{dt} \dots\dots (3)$$

Simplify the equation (2).

$$v_1 = v_0 + 2 \frac{dv_0}{dt} \dots\dots (4)$$

Step 3 of 3

Substitute the value of v_1 in equation (3).

$$\begin{aligned} \frac{v_s}{100 \times 10^3} &= \frac{v_0}{100 \times 10^3} + (40 \times 10^{-6}) \frac{dv_0}{dt} + (20 \times 10^{-6}) \frac{d^2 v_0}{dt^2} \\ \frac{d^2 v_0}{dt^2} + \frac{dv_0}{dt} + 0.5 v_0 &= 0.5 v_s \end{aligned}$$

Therefore, the required differential equation for the output voltage v_0 is

$$\boxed{\frac{d^2 v_0}{dt^2} + \frac{dv_0}{dt} + 0.5 v_0 = 0.5 v_s}$$