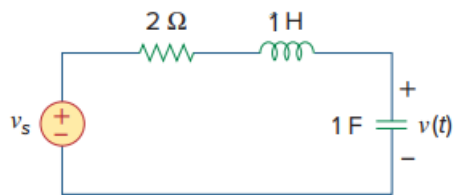


Problem

For the step function $v_s = u(t)$, use *PSpice* or *MultiSim* to find the response $v(t)$ for $0 < t < 6$ s in the circuit of Fig. 8.113.

Figure 8.113:



Step-by-step solution

Step 1 of 3


The schematic below is as shown below. The unit step is modeled by VPWL as shown. We insert a voltage marker to display V after simulation. We set print step = $25 \mu\text{S}$ & final step = 6 S in transient box. The output plot is shown below.

T1 = 0 V1 = 0

T2 = 0.001 V2 = 1

T3 = 100 V3 = 1.0

Step 2 of 3

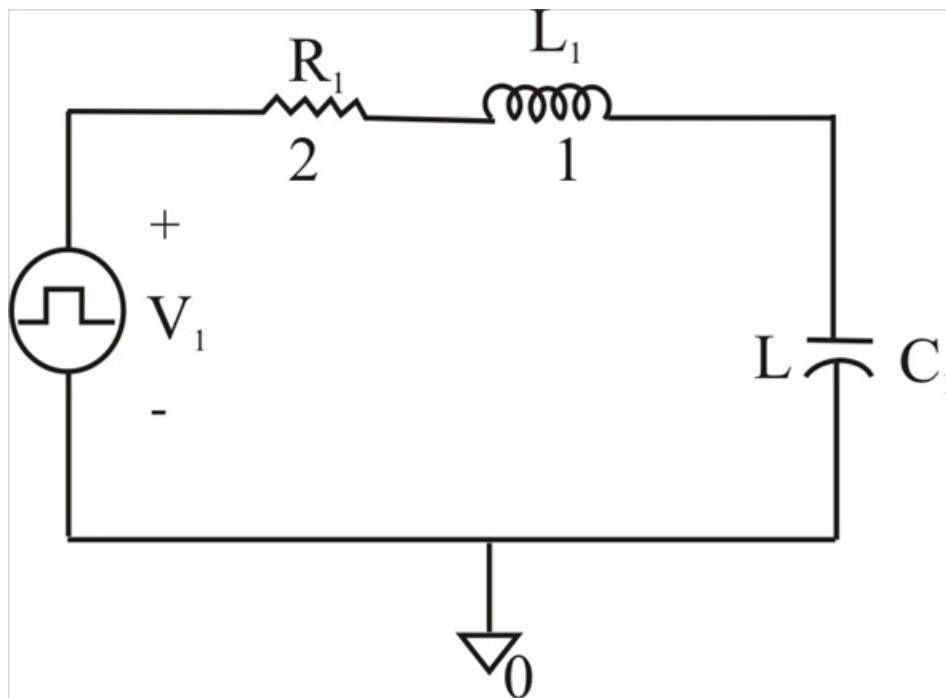

Step 3 of 3

