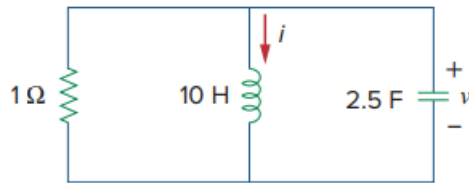


Problem

Given the source-free circuit in Fig. 8.114, use *PSpice* or *MultiSim* to get $i(t)$ for $0 < t < 20$ s. Take $v(0) = 30$ V and $i(0) = 2$ A.




Step-by-step solution

Step 1 of 3

The schematic is shown below. The initial values are as set as attributes of L1, & C1. We set print step to 25μ S and final time to 20 S in the transient box. A current marker is inserted at terminal of L1 to automatically display $i(t)$ after simulation. The result is shown below.

Step 2 of 3

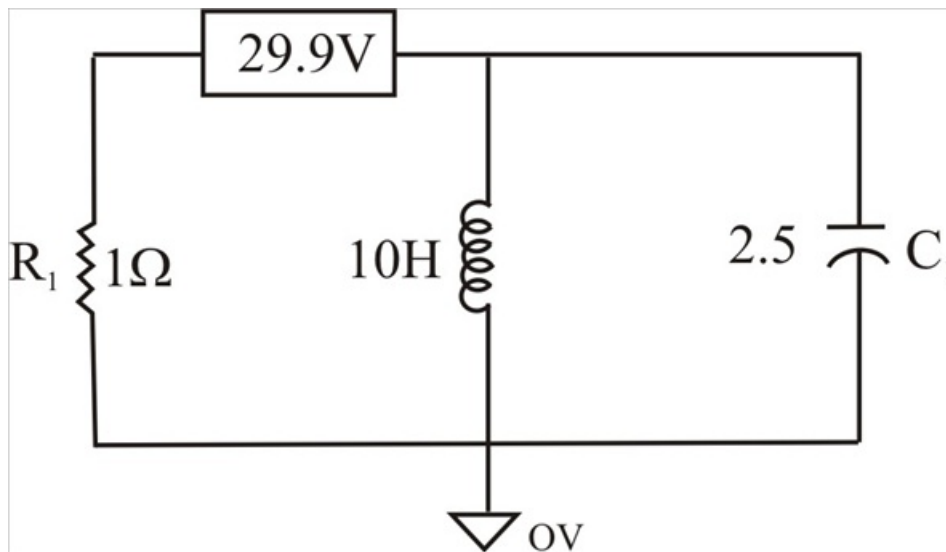

Step 3 of 3

