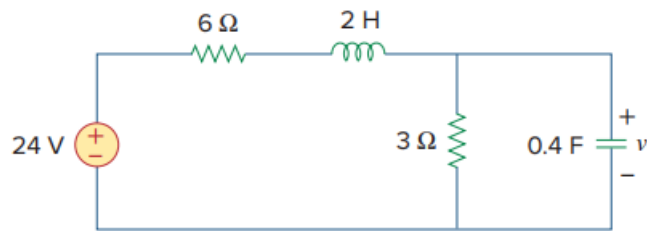


Problem


For the circuit in Fig. 8.115, use *PSpice* or *MultiSim* to obtain $v(t)$ for $0 < t < 4$ s. Assume that the capacitor voltage and inductor current at $t = 0$ are both zero.



Step-by-step solution

Step 1 of 2

The schematic is below.

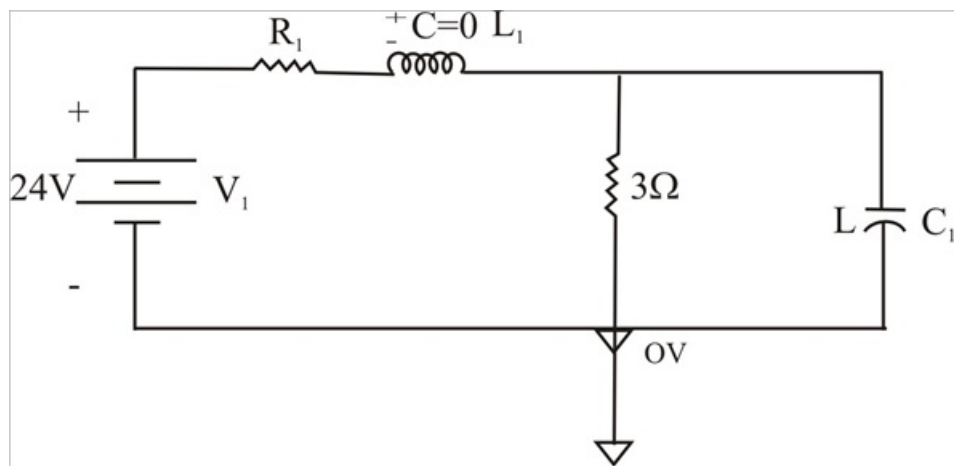

Step 2 of 2

After the circuit is saved and simulated, we obtain the capacitor voltage $V(t)$ as shown below.

