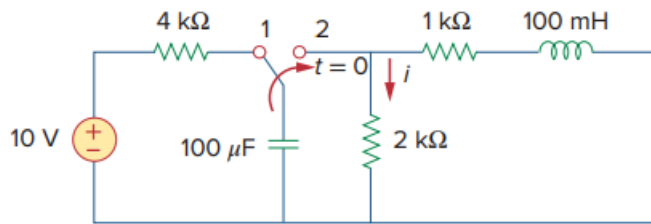


Problem

The switch in Fig. 8.117 has been in position 1 for a long time. At $t = 0$, it is switched to position 2. Use *PSpice* or *MultiSim* to find $i(t)$ for $0 < t < 0.2$ s.


Figure 8.117:



Step-by-step solution

Step 1 of 2

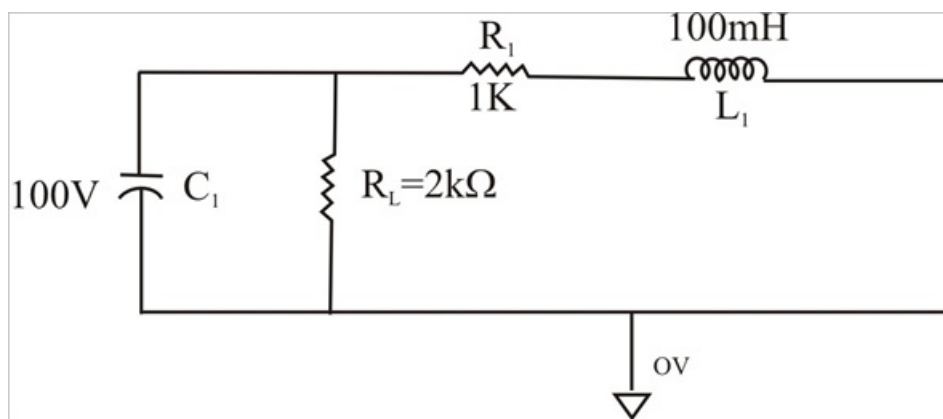When the switch is in position 1, we obtain $i_C = 10$ for the capacitor and $i_L = 0$ for the inductor. When switch is in position 2, the schematic of the circuit is shown below.



Step 2 of 2

When the circuit is simulated, we obtain $i(t)$ as shown below.

