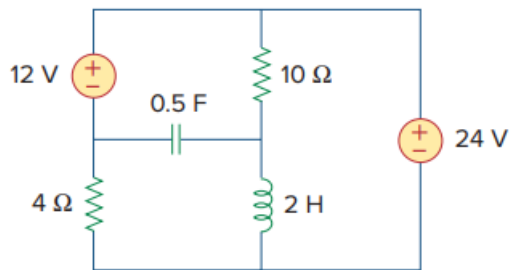


Problem

Obtain the dual of the circuit in Fig. 8.119.

Figure 8.119:



Step-by-step solution

Step 1 of 2

The dual circuit is connected as shown in fig(a) redraw in fig(a).

It is redrawn in fig(b).


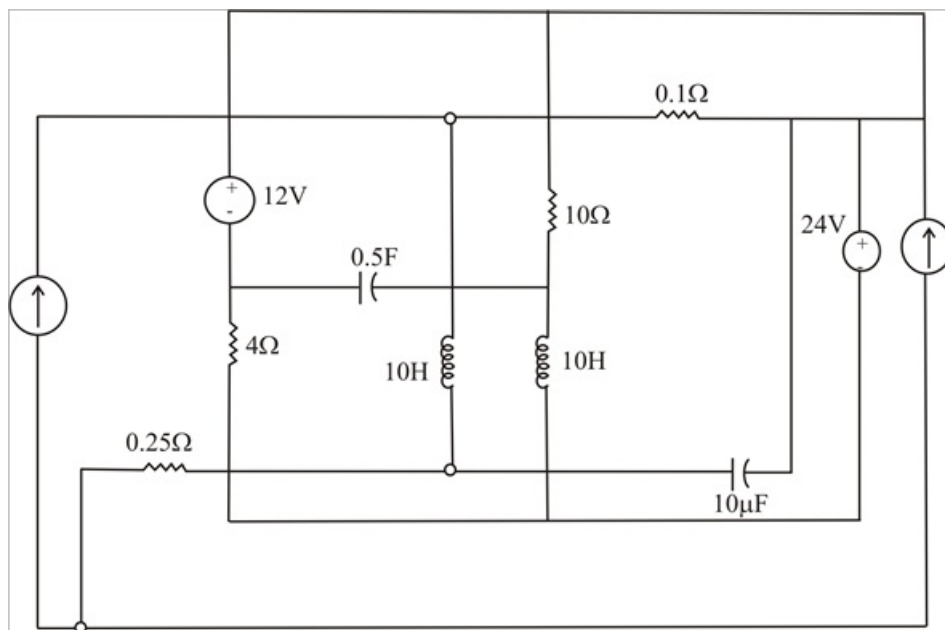


Fig (a)

Step 2 of 2

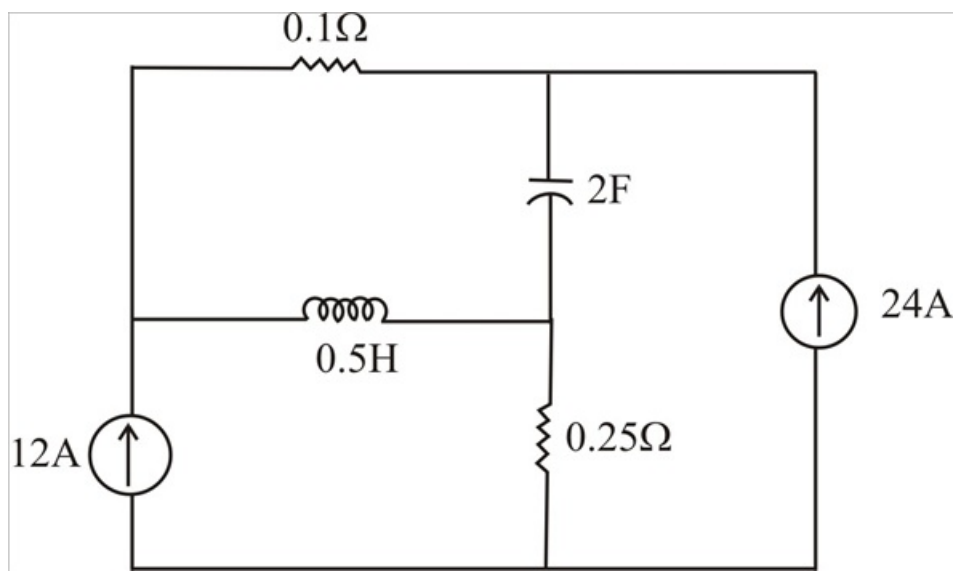

Fig(b)