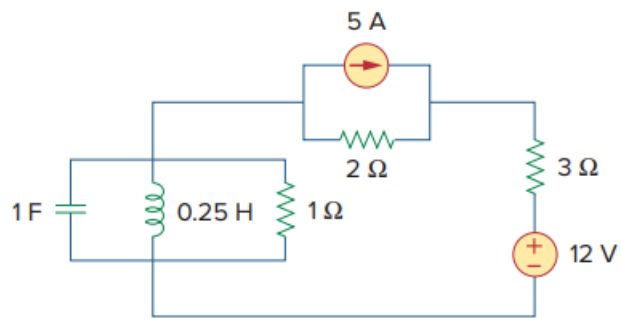


Problem

Draw the dual of the circuit in Fig. 8.121.


Figure 8.121:



Step-by-step solution

Step 1 of 2

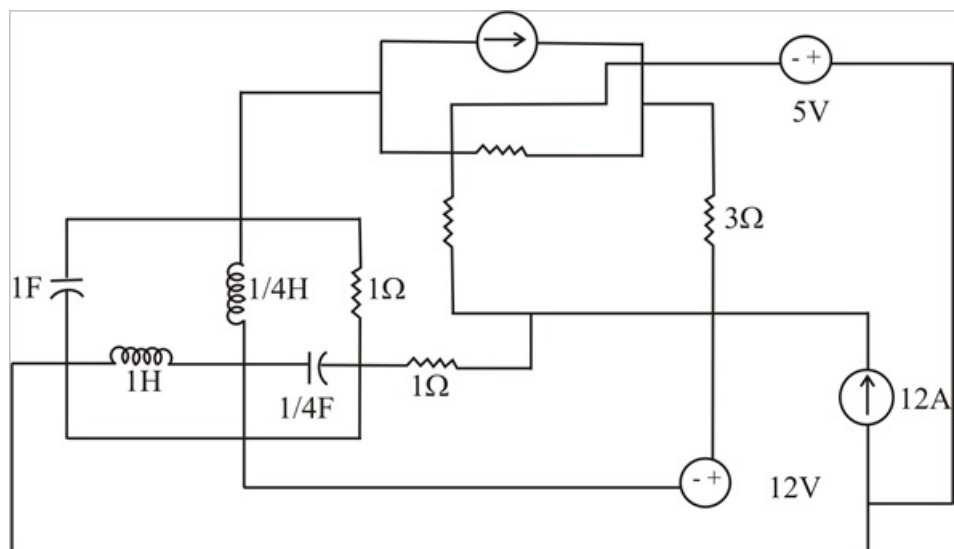The dual is construction in fig(a) & redrawn in fig(b).



Fig(a)

Step 2 of 2

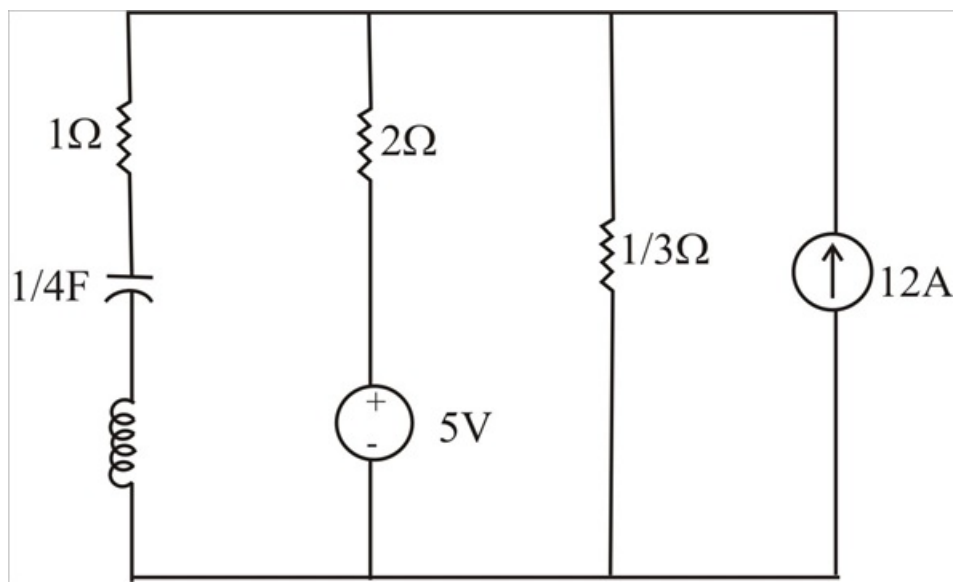


Fig (b)