

Chapter 9, Problem 8PP

Problem

If voltage $v = 25 \sin(100t - 15^\circ)$ V is applied to a $50 \mu\text{F}$ capacitor, calculate the current through the capacitor.

Step-by-step solution

Step 1 of 3

Write the given sinusoidal expression of voltage.

$$v = 25 \sin(100t - 15^\circ) \text{ V}$$

Here,

The magnitude of the voltage v_m is 25 V

The angular frequency ω is 100 rad/s

The phase angle is -15° .

The phasor representation of voltage is,

$$\mathbf{V} = 25 \angle -15^\circ \text{ V}$$

Step 2 of 3

Determine the reactance of $50 \mu\text{F}$ capacitor.

$$\begin{aligned} X_c &= \frac{1}{j\omega C} \\ &= \frac{1}{j(100)(50 \times 10^{-6})} \\ &= -j200 \\ &= 200 \angle -90^\circ \Omega \end{aligned}$$

Step 3 of 3

Calculate the current through the capacitor.

$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}}{X_c} \\ &= \frac{25 \angle -15^\circ}{200 \angle -90^\circ} \\ &= 0.125 \angle 75^\circ \text{ A} \\ &= 125 \angle 75^\circ \text{ mA} \end{aligned}$$

Convert the current expression from phasor domain to time domain.

$$\begin{aligned} i &= i_m \sin(\omega t + \phi) \\ &= 125 \sin(100t + 75^\circ) \text{ mA} \end{aligned}$$

Therefore, the current through the capacitor is $\boxed{125 \sin(100t + 75^\circ) \text{ mA}}$.