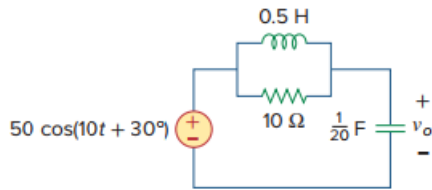


Problem

Calculate v_o in the circuit of Fig. 9.27.

Figure 9.27:



Step-by-step solution

Step 1 of 8

Find the phasor corresponding to the sinusoid $v(t) = 50 \cos(10t + 30^\circ)$ V.

$$\begin{aligned} v(t) &= 50 \cos(10t + 30^\circ) \text{ V} \\ &= 50 \angle 30^\circ \text{ V} \end{aligned}$$

Therefore, the phasor $\mathbf{V}_s$ corresponding to sinusoid $v(t) = 50 \cos(10t + 30^\circ)$ V is $50 \angle 30^\circ$ V.

Calculate the value of the impedance $\mathbf{Z}_C$ of the $\frac{1}{20}$ F capacitor at $\omega = 10$ rad/s.

Write the expression for the impedance $\mathbf{Z}_C$ of the $\frac{1}{20}$ F capacitor at $\omega = 10$ rad/s.

$$\begin{aligned} \mathbf{Z}_C &= \frac{-j}{\omega C} \\ \mathbf{Z}_C &= \frac{-j}{10 \left(\frac{1}{20} \right)} \\ &= -j2 \end{aligned}$$

Therefore, the value of impedance $\mathbf{Z}_C$ of the $\frac{1}{20}$ F capacitor at $\omega = 10$ rad/s is $-j2 \Omega$.

Step 2 of 8

Calculate the value of the impedance $\mathbf{Z}_L$ of the 0.5 H inductor at $\omega = 10$ rad/s.

Write the expression for the impedance $\mathbf{Z}_L$ of the 0.5 H inductor at $\omega = 10$ rad/s.

$$\begin{aligned} \mathbf{Z}_L &= j\omega L \\ \mathbf{Z}_L &= j10(0.5) \\ &= j5 \end{aligned}$$

Therefore, the value of impedance $\mathbf{Z}_L$ of the 0.5 H inductor at $\omega = 10$ rad/s is $j5 \Omega$.

Step 3 of 8

Draw the phasor domain equivalent circuit of Figure 1 as shown in Figure 2.

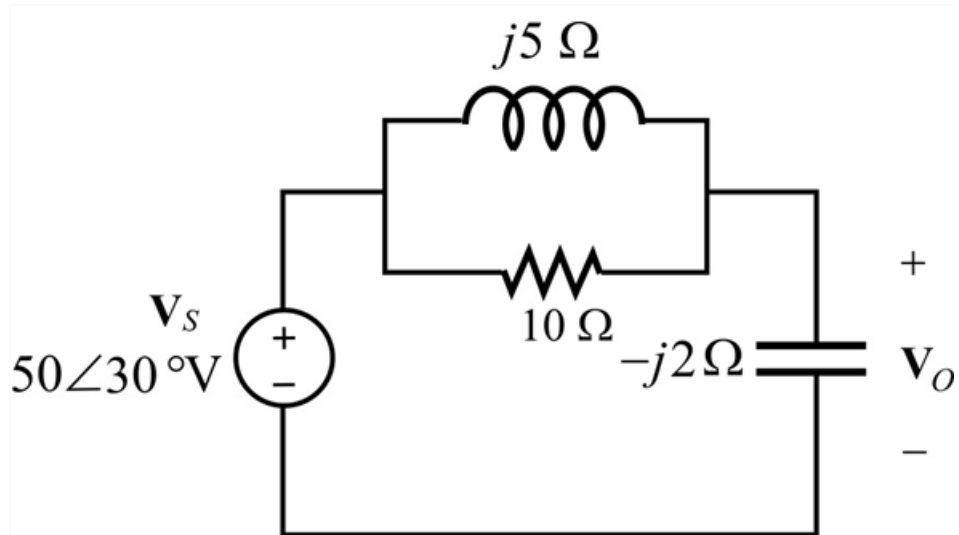


Figure 2: Phasor domain equivalent circuit.

Step 4 of 8

Consider Z_1 is the impedance of the 0.5 H inductor in parallel with the resistor 10Ω .

Z_2 is the impedance of the $\frac{1}{20} \text{ F}$ capacitor.

Redraw the Figure 1 as shown in Figure 2 for analysis.

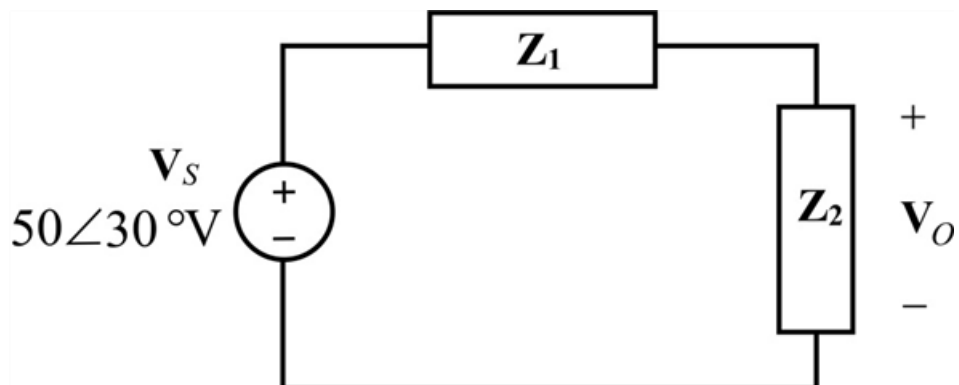


Figure 3: Simplified Phasor domain equivalent circuit.

Step 5 of 8

Calculate the value of $\mathbf{Z}_1$.

Write the expression for $\mathbf{Z}_1$.

$$\begin{aligned}\mathbf{Z}_1 &= \mathbf{Z}_L \parallel 10 \\ &= \frac{\mathbf{Z}_L(10)}{\mathbf{Z}_L + 10}\end{aligned}$$

Substitute $j5\ \Omega$ for $\mathbf{Z}_L$ in this expression.

$$\begin{aligned}\mathbf{Z}_1 &= \frac{j5(10)}{j5 + 10} \\ &= \frac{j50}{j5 + 10} \\ &= \left(\frac{j10}{2 + j} \right) \\ &= (2 + j4)\ \Omega\end{aligned}$$

Therefore, the value of $\mathbf{Z}_1$ is $(2 + j4)\ \Omega$.

Step 6 of 8

Calculate the value of the output voltage $\mathbf{V}_o$.

Apply voltage division rule across the impedance $\mathbf{Z}_2$ to find the output voltage $\mathbf{V}_o$.

$$\mathbf{V}_o = \frac{\mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} \mathbf{V}_s$$

Substitute $(2 + j4)\ \Omega$ for $\mathbf{Z}_1$, $-j2\ \Omega$ for $\mathbf{Z}_2$ in this expression.

$$\begin{aligned}\mathbf{V}_o &= \frac{-j2}{2 + j4 - j2} 50\angle 30^\circ \\ &= \frac{-j2}{2 + j2} 50\angle 30^\circ \\ &= \frac{-j}{1 + j} 50\angle 30^\circ \\ &= (-0.5 - j0.5) 50\angle 30^\circ\end{aligned}$$

Step 7 of 8

Simplify $\mathbf{V}_o$ further.

$$\mathbf{V}_o = 35.36\angle -105^\circ$$

Therefore, the value of the output voltage $\mathbf{V}_o$ in phasor form is $35.36\angle -105^\circ\ \text{V}$.

Step 8 of 8

Find the sinusoid corresponding to the phasor output voltage $\mathbf{V}_o = 35.36\angle -105^\circ\ \text{V}$

$$\mathbf{V}_o = 35.36\angle -105^\circ\ \text{V}$$

$$v_o(t) = 35.36 \cos(10t - 105^\circ)\ \text{V}$$

Therefore, the value of the required output voltage $v_o(t)$ is $\boxed{35.36 \cos(10t - 105^\circ)\ \text{V}}$.