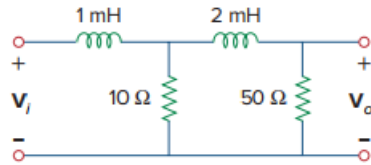


Problem

Refer to the RL circuit in Fig. 9.36. If 10 V is applied to the input, find the magnitude and the phase shift produced at 5 kHz. Specify whether the phase shift is leading or lagging.

Figure 9.36:



Step-by-step solution

Step 1 of 6

Calculate the value of the angular frequency ω .

Write the expression for the angular frequency ω .

$$\begin{aligned}\omega &= 2\pi f \\ &= 2(3.14)(5 \times 10^3) \\ &= 31415.9 \text{ rad/s}\end{aligned}$$

Therefore, the value of the angular frequency ω is 31415.9 rad/s.

Consider Z_1 is the impedance of the 1 mH inductor.

Z_2 is the impedance of the resistor 10Ω .

Z_3 is the impedance of the 2 mH inductor in series with the resistor 50Ω .

Redraw the Figure 1 as shown in Figure 2 for finding Z_{in} at $\omega = 31415.9 \text{ rad/s}$.

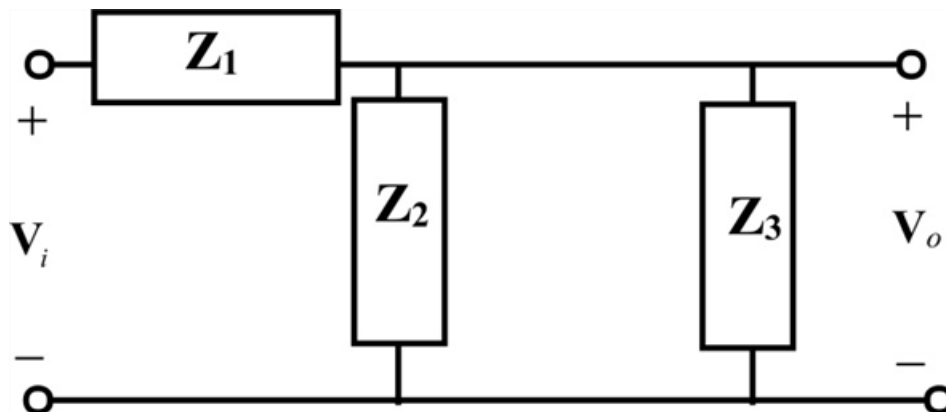


Figure 2

Step 2 of 6

Calculate the value of $\mathbf{Z}_1$.

Write the expression for $\mathbf{Z}_1$.

$$\mathbf{Z}_1 = j\omega L$$

Substitute 31415.9 rad/s for ω , 1×10^{-3} for L in this expression.

$$\begin{aligned}\mathbf{Z}_1 &= j(31415.9)1 \times 10^{-3} \\ &= j31.42\end{aligned}$$

Therefore, the value of $\mathbf{Z}_1$ is $j31.42 \Omega$.

Step 3 of 6

Calculate the value of $\mathbf{Z}_2$.

Write the expression for $\mathbf{Z}_2$.

$$\mathbf{Z}_2 = 10 \Omega$$

Therefore, the value of $\mathbf{Z}_2$ is 10Ω .

Step 4 of 6

Calculate the value of $\mathbf{Z}_3$.

Write the expression for $\mathbf{Z}_3$.

$$\mathbf{Z}_3 = j\omega L + 50$$

Substitute 31415.9 rad/s for ω , 2×10^{-3} for L in this expression.

$$\begin{aligned}\mathbf{Z}_3 &= j(31415.9)(2 \times 10^{-3}) + 50 \\ &= j62.84 + 50 \\ &= (50 + j62.84)\end{aligned}$$

Therefore, the value of $\mathbf{Z}_3$ is $(50 + j62.84) \Omega$.

Step 5 of 6

Calculate the value of the impedance $\mathbf{Z}_2 \parallel \mathbf{Z}_3$.

Write the expression for the impedance $\mathbf{Z}_2 \parallel \mathbf{Z}_3$.

$$\begin{aligned}\mathbf{Z}_2 \parallel \mathbf{Z}_3 &= \frac{\mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_2 + \mathbf{Z}_3} \\ &= \frac{10(50 + j62.84)}{(10 + 50 + j62.84)} \\ &= (9.205 + j0.832)\end{aligned}$$

Therefore, the value of $\mathbf{Z}_2 \parallel \mathbf{Z}_3$ is $(9.205 + j0.832) \Omega$.

Calculate the value of the output voltage $\mathbf{V}_{o1}$.

Apply voltage division rule across the impedance $\mathbf{Z}_2 \parallel \mathbf{Z}_3$ to find the output voltage $\mathbf{V}_{o1}$.

$$\begin{aligned}\mathbf{V}_{o1} &= \frac{\mathbf{Z}_2 \parallel \mathbf{Z}_3}{\mathbf{Z}_1 + \mathbf{Z}_2 \parallel \mathbf{Z}_3} \mathbf{V}_i \\ &= \frac{(9.205 + j0.832)}{(j31.42 + 9.205 + j0.832)} (10) \\ &= \frac{(9.205 + j0.832)}{(9.205 + j32.252)} (10) \\ &= (0.99 - j2.57)\end{aligned}$$

$$\mathbf{V}_{o1} = 2.755 \angle -68.9^\circ \text{ V}$$

Therefore, the value of $\mathbf{V}_{o1}$ is $2.755 \angle -68.9^\circ \text{ V}$.

Step 6 of 6

Calculate the value of the output voltage $\mathbf{V}_o$.

Apply voltage division rule across the resistor 50Ω in $\mathbf{Z}_3$ to find the output voltage $\mathbf{V}_o$.

$$\begin{aligned}\mathbf{V}_o &= \frac{50}{(50 + j62.84)} \mathbf{V}_{o1} \\ &= 0.622 \angle -51.49^\circ (2.755 \angle -68.9^\circ \text{ V}) \\ &= (0.622 \times 2.755) \angle -(51.49^\circ + 68.9^\circ) \text{ V} \\ &\cong 1.7161 \angle -120.39^\circ \text{ V}\end{aligned}$$

Therefore, the value of output voltage $\mathbf{V}_o$ is $1.7161 \angle -120.39^\circ \text{ V}$.

Hence, the magnitude and phase of the output voltage $\mathbf{V}_o$ is $\boxed{1.7161 \text{ V}}$ and $\boxed{\angle -120.39^\circ}$.

Clearly from the expression of the output voltage $\mathbf{V}_o$, the output voltage $\boxed{\text{lags}}$ the input voltage.