

Problem

A voltage $v(t) = 100 \cos(60t + 20^\circ)$ V is applied to a parallel combination of a 40-k Ω resistor and a 50- μ F capacitor. Find the steady-state currents through the resistor and the capacitor.

Step-by-step solution

Step 1 of 4

Express the applied voltage $v(t)$ in phasor domain.

$$V = 100 \angle 20^\circ \text{ V}$$

Calculate the impedance offered by the capacitor.

$$\begin{aligned} Z_c &= \frac{1}{j\omega C} \\ &= \frac{1}{j(60)(50 \times 10^{-6})} \\ &= \frac{1}{j(3 \times 10^{-3})} \\ &= -j \frac{1000}{3} \Omega \end{aligned}$$

Draw the equivalent circuit as shown in Figure 1.

Step 2 of 4

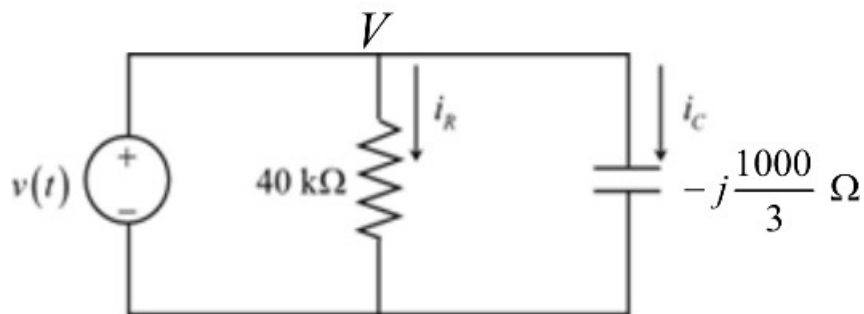


Figure: 1

Step 3 of 4

Determine the current passing through the resistor.

$$\begin{aligned} I_R &= \frac{V}{R} \\ &= \frac{100\angle 20^\circ}{40 \times 10^3} \\ &= (2.5 \times 10^3) \angle 20^\circ \\ &= 2.5 \angle 20^\circ \text{ mA} \end{aligned}$$

Express the current passing through the resistor in time domain.

$$i_c(t) = 2.5 \cos(60t + 20^\circ) \text{ mA}$$

Thus, the steady state current passing through the resistor is $\boxed{2.5 \cos(60t + 20^\circ) \text{ mA}}$.

Step 4 of 4

Determine the current passing through the capacitor.

$$\begin{aligned} I_C &= \frac{V}{Z_C} \\ &= \frac{100\angle 20^\circ}{-j \frac{1000}{3}} \\ &= \frac{100\angle 20^\circ}{\frac{1000}{3} \angle -90^\circ} \\ &= 0.3 \angle (90^\circ + 20^\circ) \text{ A} \end{aligned}$$

Express the current passing through the capacitor in time domain.

$$\begin{aligned} i_c(t) &= 0.3 \cos(60t + 90^\circ + 20^\circ) \\ &= 0.3 \cos(90^\circ + (60t + 20^\circ)) \\ &= -0.3 \sin(60t + 20^\circ) \\ &= -300 \sin(60t + 20^\circ) \text{ mA} \end{aligned}$$

Thus, the steady state current passing through the capacitor is $\boxed{-300 \sin(60t + 20^\circ) \text{ mA}}$.