

Chapter 9, Problem 33P

Problem

A series RL circuit is connected to a 220-V ac source. If the voltage across the resistor is 170 V, find the voltage across the inductor.

Step-by-step solution

Step 1 of 2

The source voltage in a series RL circuit can be expressed as the sum of the magnitudes of voltage across resistor and inductor, mathematically it can be written as follows:

$$|\mathbf{V}_S| = |\mathbf{V}_R| + |\mathbf{V}_L|$$

$$\mathbf{V}_S^2 = \mathbf{V}_R^2 + \mathbf{V}_L^2$$

$$\mathbf{V}_L^2 = \mathbf{V}_S^2 - \mathbf{V}_R^2$$

$$\mathbf{V}_L = \sqrt{\mathbf{V}_S^2 - \mathbf{V}_R^2}$$

Step 2 of 2

Substitute 220 V for $\mathbf{V}_S$ and 170 V for $\mathbf{V}_R$.

$$\begin{aligned}\mathbf{V}_L &= \sqrt{\mathbf{V}_S^2 - \mathbf{V}_R^2} \\ &= \sqrt{(220)^2 - (170)^2} \\ &= 139.64 \text{ V}\end{aligned}$$

Therefore, the voltage across the inductor is 139.64 V.