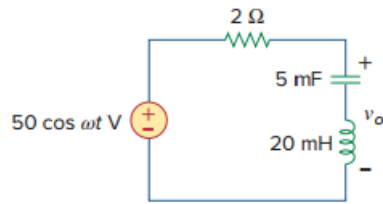


Problem


What value of ω will cause the forced response, v_o , in Fig. 9.41 to be zero?

Figure 9.41:



Step-by-step solution

Step 1 of 3

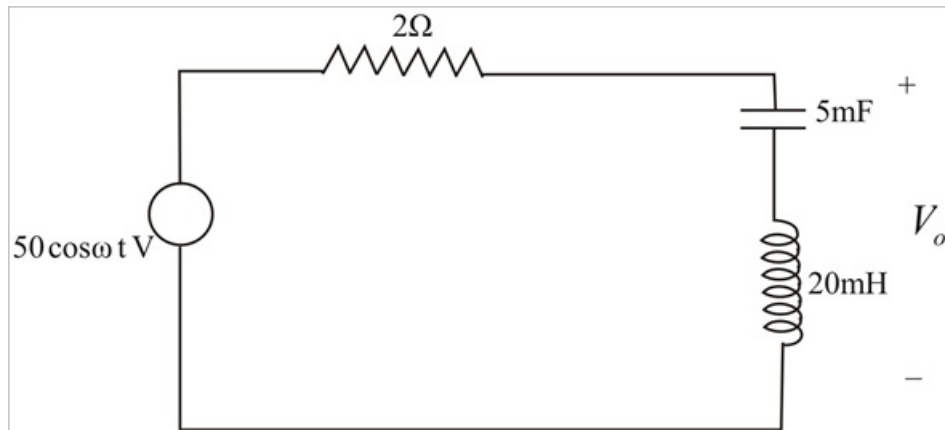

Step 2 of 3

$$\begin{aligned}
 V &= 50 \cos \omega t = 50 \angle 0^\circ \\
 Z_1 &= 2 \Omega \\
 Z_2 &= \frac{1}{j\omega C} + j\omega L \\
 &= \frac{-j}{\omega \times 5 \times 10^{-3}} + j\omega(20 \times 10^{-3}) \\
 &= \frac{-j}{\omega} 0.2 \times 10^3 + j\omega(20 \times 10^{-3}) \\
 V_o &= \frac{Z_2}{Z_1 + Z_2} V \\
 &= \frac{\frac{-j}{\omega} (0.2 \times 10^3) + j\omega(20 \times 10^{-3})}{\frac{-j}{\omega} (0.2 \times 10^3) + j\omega(20 \times 10^{-3}) + 2} \{50 \angle 0^\circ\}
 \end{aligned}$$

Step 3 of 3

For V_0 to be zero,

$$\frac{-j}{\omega}(0.2 \times 10^3) + j\omega(20 \times 10^{-3}) = 0$$

$$-j(0.2 \times 10^3) + j\omega^2(20 \times 10^{-3}) = 0$$

$$0.2 \times 10^3 = \omega^2(20 \times 10^{-3})$$

$$\omega^2 = \frac{0.2 \times 10^3}{20 \times 10^{-3}} = 0.01 \times 10^6 = 10000$$

$$\omega = 100 \text{ Hz} .$$