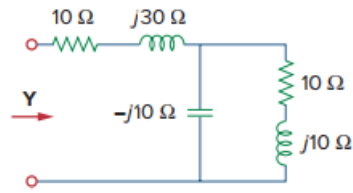


Problem

Determine the admittance $\mathbf{Y}$ for the circuit in Fig. 9.44.

Figure 9.44:



Step-by-step solution

Step 1 of 2

Refer to Figure 9.44 in the text book for the circuit.

Determine the impedance of the network.

$$\begin{aligned} \mathbf{Z} &= (10 + j30) + (-j10) \parallel (10 + j10) \\ &= (10 + j30) + \frac{(-j10) \times (10 + j10)}{(-j10) + (10 + j10)} \\ &= 10 + j30 + 10 - j10 \\ &= 20 + j20 \, \Omega \end{aligned}$$

Step 2 of 2

The admittance $\mathbf{Y}$ is defined as the reciprocal of the impedance.

Determine the admittance $\mathbf{Y}$.

$$\begin{aligned} \mathbf{Y} &= \frac{1}{\mathbf{Z}} \\ &= \frac{1}{20 + j20} \\ &= 0.025 - j0.025 \\ &= (25 - j25) \times 10^{-3} \, \text{S} \\ &= (25 - j25) \, \text{mS} \end{aligned}$$

Thus, the admittance $\mathbf{Y}$ of the circuit is $\boxed{(25 - j25) \, \text{mS}}$.