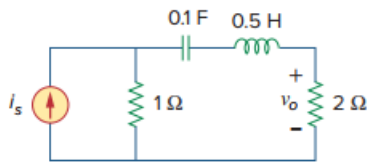


Problem

If the voltage v_o across the $2\text{-}\Omega$ resistor in the circuit of Fig. 9.58 is $90 \cos 2t$ V, obtain i_s .

Figure 9.58:



Step-by-step solution

Step 1 of 6

Refer to Figure 9.58 in the text book.

Consider the value of the voltage $v_o(t)$.

$$v_o(t) = 90 \cos 2t \text{ V}$$

Represent in phasor form.

$$\mathbf{V}_o = 90 \angle 0^\circ \text{ V}$$

Therefore, the value of the voltage in phasor form is $90 \angle 0^\circ \text{ V}$.

Step 2 of 6

Calculate the value of the reactance due to inductance.

$$X_L = j\omega L$$

Substitute 2 rad/s for ω and 0.5 H for L .

$$\begin{aligned} X_L &= j(2)(0.5) \\ &= j1 \\ &= 1 \angle 90^\circ \Omega \end{aligned}$$

Therefore, the value of the reactance X_L is $1 \angle 90^\circ \Omega$.

Step 3 of 6

Calculate the value of the reactance due to capacitance.

$$X_C = \frac{1}{j\omega C}$$

Substitute 2 rad/s for ω and 0.1 F for C .

$$\begin{aligned} X_C &= \frac{1}{j(2)(0.1)} \\ &= \frac{1}{j0.2} \\ &= 5 \angle -90^\circ \Omega \end{aligned}$$

Therefore, the value of the reactance X_C is $5 \angle -90^\circ \Omega$.

Step 4 of 6

Draw the circuit diagram in phasor representation.

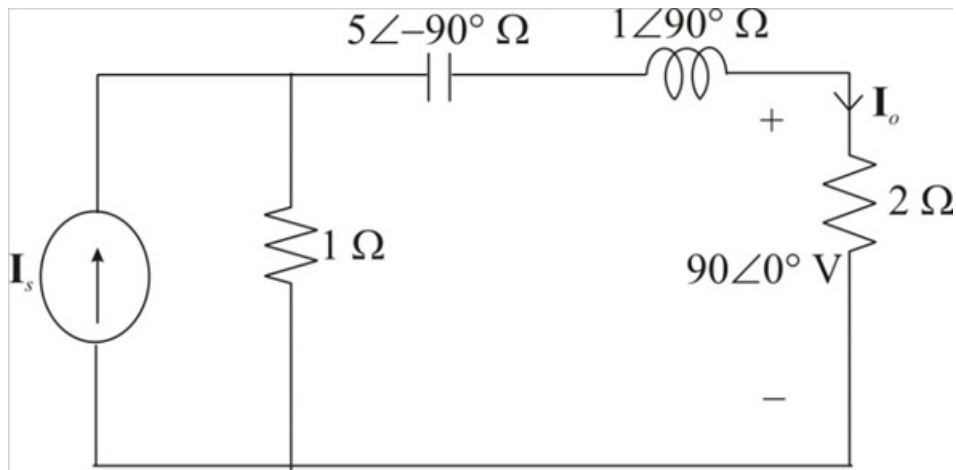


Figure 1

Step 5 of 6

Calculate the value of the current I_o .

$$I_o = \frac{V_o}{2}$$

Substitute $90\angle 0^\circ\text{ V}$ for V_o .

$$I_o = \frac{90\angle 0^\circ}{2}$$

$$= 45\angle 0^\circ\text{ A}$$

Therefore, the value of the current I_o is $45\angle 0^\circ\text{ A}$.

Step 6 of 6

Write the expression for the current I_o using current divider rule.

$$I_o = I_s \left(\frac{1}{1 + (1\angle 90^\circ + 5\angle -90^\circ + 2)} \right)$$

Substitute $45\angle 0^\circ\text{ A}$ for I_o .

$$45\angle 0^\circ = I_s \left(\frac{1}{5\angle -53.13^\circ} \right)$$

$$45\angle 0^\circ = I_s (0.2\angle 53.13^\circ)$$

$$I_s = \frac{45\angle 0^\circ}{0.2\angle 53.13^\circ}$$

$$I_s = 225\angle -53.13^\circ\text{ A}$$

Represent in time domain.

$$i_s(t) = 225\cos(2t - 53.13^\circ)\text{ A}$$

Therefore, the value of the current $i_s(t)$ is $225\cos(2t - 53.13^\circ)\text{ A}$.