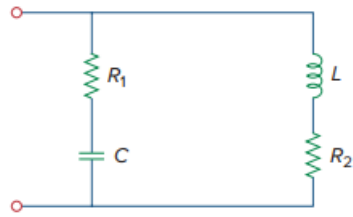


Problem

Using Fig. 9.65, design a problem to help other students better understand impedance combinations.


Figure 9.65:



Step-by-step solution

Step 1 of 2

Given circuit can be represented as

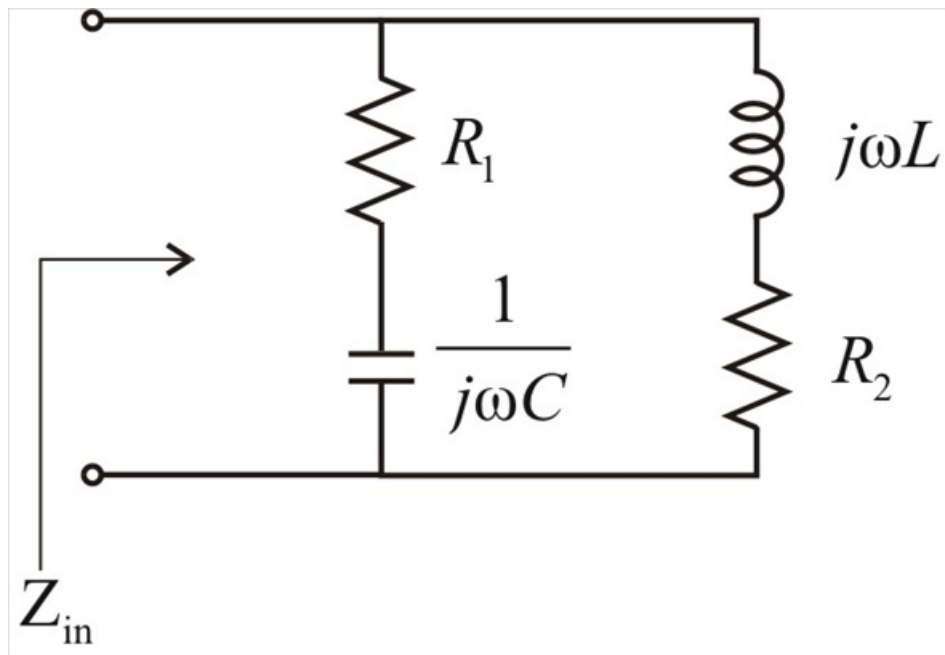

Step 2 of 2

From the above circuit,

$$Z_{in} = \left(R_1 + \frac{1}{j\omega C} \right) \parallel (j\omega L + R_2)$$

$$Z_{in} = \left(\frac{j\omega R_1 C + 1}{j\omega C} \right) \parallel (j\omega L + R_2)$$

$$Z_{in} = \frac{\frac{(j\omega R_1 C + 1)}{j\omega C} \times (j\omega L + R_2)}{\left(\frac{j\omega R_1 C + 1}{j\omega C} \right) + (j\omega L + R_2)}$$

$$Z_{in} = \frac{(j\omega R_1 C + 1)(j\omega L + R_2)}{(j\omega R_1 C + 1) + (j\omega L + R_2)(j\omega C)}$$

$$Z_{in} = \frac{(-\omega^2 R_1 LC + j\omega L + j\omega R_1 R_2 C + R_2)}{j\omega R_1 C + 1 - \omega^2 LC + j\omega R_2 C}$$

$$\therefore Z_{in} = \frac{j\omega(L + R_1 R_2 C) - \omega^2 R_1 LC + R_2}{1 - \omega^2 LC + j\omega C(R_1 + R_2)}$$