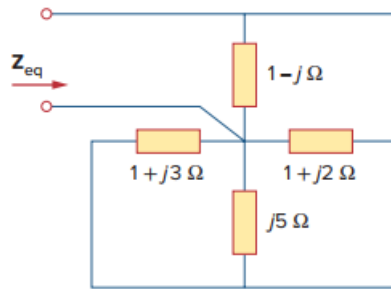


Problem

Find Z_{eq} in the circuit of Fig. 9.68.

Figure 9.68:



Step-by-step solution

Step 1 of 1

All of the Impedances are in parallel,

$$\begin{aligned} \frac{1}{Z_{eq}} &= \frac{1}{1-j} + \frac{1}{1+j2} + \frac{1}{j5} + \frac{1}{1+j3} \\ \frac{1}{Z_{eq}} &= (0.5+j0.5) + (0.2-j0.4) + (-j0.2) + (0.1-j0.3) \\ &= 0.8 - j0.4 \\ Z_{eq} &= \frac{1}{0.8-j0.4} = 1 + j0.5 \Omega . \end{aligned}$$