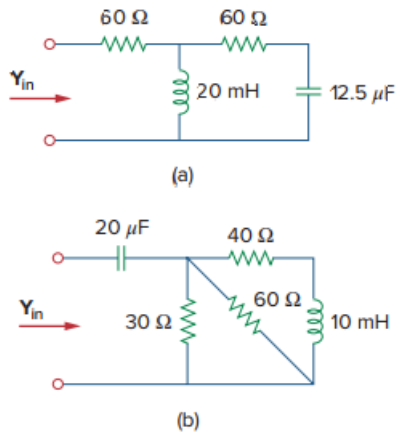


Problem

At $\omega = 103 \text{ rad/s}$, find the input admittance of each of the circuits in Fig. 9.74.

Figure 9.74:



Step-by-step solution

Step 1 of 6

Refer to figure 9.74 given in the textbook.

(a)

Calculate the impedance of inductor Z_L .

$$Z_L = j\omega L$$

Substitute 10^3 for ω , and 20×10^{-3} for L .

$$Z_L = j \times 10^3 \times 20 \times 10^{-3}$$

$$Z_L = j20 \Omega$$

Calculate the impedance of capacitor Z_C .

$$Z_C = \frac{1}{j\omega C}$$

Substitute 10^3 for ω , and 12.5×10^{-6} for C .

$$Z_C = \frac{1}{j \times 10^3 \times 12.5 \times 10^{-6}}$$

$$Z_C = -j80 \Omega$$

Step 2 of 6

Calculate the impedance seen from the same end from which the admittance is seen.

$$Z_{in} = 60 + [(Z_L) \parallel (60 + Z_C)]$$

Substitute $j20$ for Z_L , and $-j80$ for Z_C .

$$\begin{aligned} Z_{in} &= 60 + [(j20) \parallel (60 - j80)] \\ &= 60 + \frac{j20 \times (60 - j80)}{j20 + 60 - j80} \\ &= 60 + \frac{j1200 + 1600}{60 - j60} \\ &= (63.333 + j23.333) \Omega \end{aligned}$$

Step 3 of 6

Calculate the admittance Y_{in} .

$$Y_{in} = \frac{1}{Z_{in}}$$

Substitute $(63.333 + j23.333)$ for Z_{in} .

$$\begin{aligned} Y_{in} &= \frac{1}{(63.333 + j23.333)} \\ &= (0.014) - j(0.005122) \\ &= 0.0148 \angle -20.22^\circ \\ &= 14.8 \angle -20.22^\circ \text{ mS} \end{aligned}$$

Therefore, the admittance Y_{in} is $14.8 \angle -20.22^\circ \text{ mS}$.

Step 4 of 6

(b)

Calculate the impedance of inductor Z_L .

$$Z_L = j\omega L$$

Substitute 10^3 for ω , and 10×10^{-3} for L .

$$\begin{aligned} Z_L &= j \times 10^3 \times 10 \times 10^{-3} \\ &= j10 \Omega \end{aligned}$$

Calculate the impedance of capacitor Z_C .

$$Z_C = \frac{1}{j\omega C}$$

Substitute 10^3 for ω , and 20×10^{-6} for C .

$$\begin{aligned} Z_C &= \frac{1}{j \times 10^3 \times 20 \times 10^{-6}} \\ &= -j50 \Omega \end{aligned}$$

Step 5 of 6

Calculate the impedance seen from the same end from which the admittance is seen.

$$Z_{in} = Z_C + [30 \parallel 60 \parallel (40 + Z_L)]$$

Substitute $j10$ for Z_L , and $-j50$ for Z_C .

$$Z_{in} = -j50 + [20 \parallel (40 + j10)]$$

$$Z_{in} = -j50 + \left[\frac{20 \times (40 + j10)}{20 + 40 + j10} \right]$$

$$Z_{in} = -j50 + \left[\frac{800 + j200}{60 + j10} \right]$$

$$Z_{in} = -j50 + 13.5135 + j1.081$$

$$Z_{in} = (13.51 - j48.92) \Omega$$

Step 6 of 6

Calculate the admittance Y_{in} .

$$Y_{in} = \frac{1}{Z_{in}}$$

Substitute $(13.51 - j48.92)$ for Z_{in} .

$$\begin{aligned} Y_{in} &= \frac{1}{(13.51 - j48.92)} \\ &= (5.2466 \times 10^{-3}) + j0.1899 \\ &= 19.704 \angle 74.55^\circ \text{ mS} \end{aligned}$$

Therefore, the admittance Y_{in} is $\boxed{19.704 \angle 74.55^\circ \text{ mS}}$.