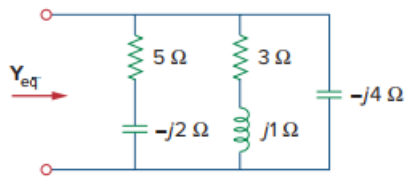


Problem

Determine Y_{eq} for the circuit in Fig. 9.75.

Figure 9.75:



Step-by-step solution

Step 1 of 1

$$Y_{eq} = \frac{1}{5 - j2} + \frac{1}{3 + j} + \frac{1}{-j4}$$

$$Y_{eq} = (0.1724 + j0.069) + (0.3 - j0.1) + (j0.25)$$

$$Y_{eq} = 0.4724 + j0.219 \text{ S}$$