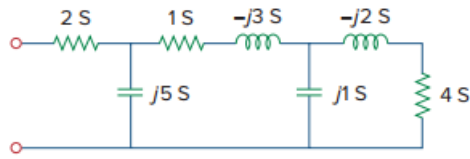


Problem

Find the equivalent admittance Y_{eq} of the circuit in Fig. 9.76.

Figure 9.76:




Step-by-step solution

Step 1 of 8

Refer to Figure 9.76 in the textbook.

Draw the circuit diagram.

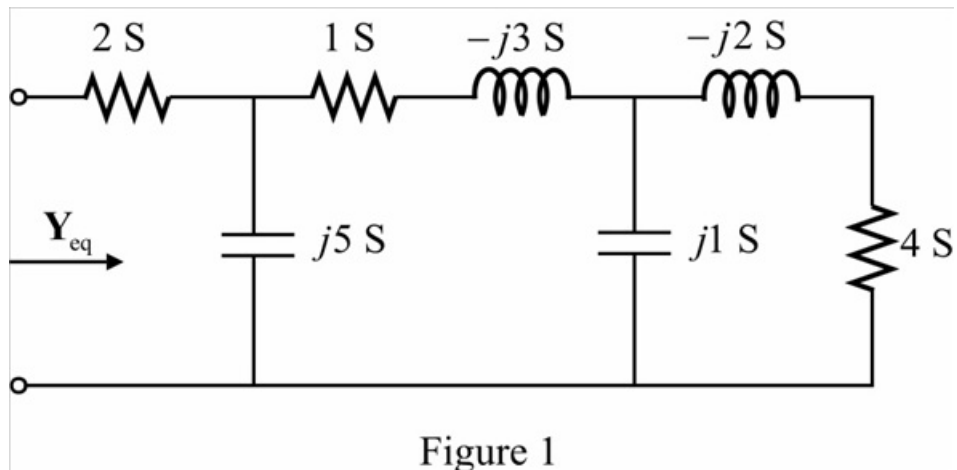

Step 2 of 8

From Figure 1, $-j2\text{ S}$ and 4 S are connected in series.

Calculate the equivalent admittance.

$$\begin{aligned}\frac{1}{Y_1} &= \frac{1}{-j2} + \frac{1}{4} \\ &= \frac{(4) + (-j2)}{(4)(-j2)} \\ Y_1 &= \frac{-j8}{4 - j2} \\ &= 0.8 - j1.6\text{ S}\end{aligned}$$

Step 3 of 8

Draw the modified circuit diagram.

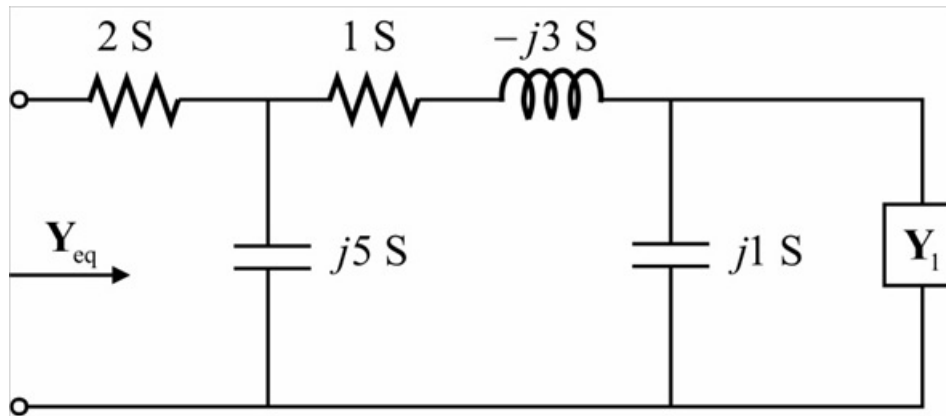


Figure 2

Step 4 of 8

From Figure 2, $j1\text{ S}$ and Y_1 are connected in parallel.

Calculate the equivalent admittance.

$$\begin{aligned} Y_2 &= (j1) + Y_1 \\ &= j1 + 0.8 - j1.6 \\ &= 0.8 - j0.6 \end{aligned}$$

Draw the modified circuit diagram.

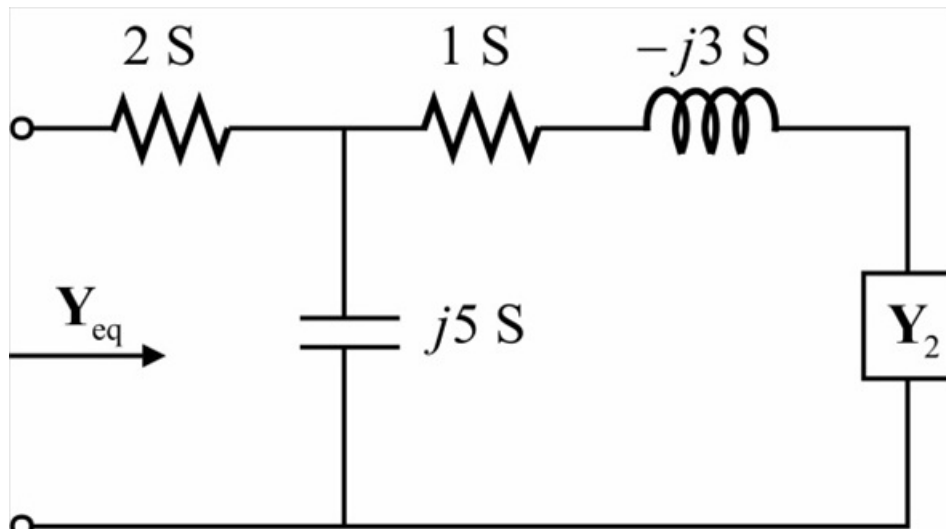


Figure 3

Step 5 of 8

From Figure 3, 1 S , $-j3\text{ S}$ and $\mathbf{Y}_2$ are connected in series.

Calculate the equivalent admittance.

$$\begin{aligned}\frac{1}{\mathbf{Y}_3} &= \frac{1}{1} + \frac{1}{-j3} + \frac{1}{\mathbf{Y}_2} \\ &= \frac{1}{1} + \frac{1}{-j3} + \frac{1}{0.8 - j0.6} \\ &= 1 + j0.334 + 0.8 + j0.6 \\ &= 1.8 + j0.934\end{aligned}$$

$$\begin{aligned}\mathbf{Y}_3 &= \frac{1}{1.8 + j0.934} \\ &= 0.4378 - j0.227\text{ S}\end{aligned}$$

Step 6 of 8

Draw the modified circuit diagram.

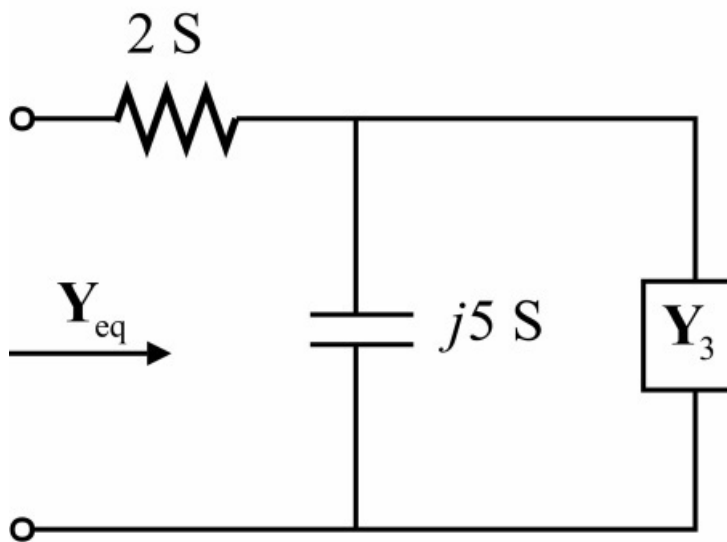


Figure 4

Step 7 of 8

From Figure 4, $j5 \text{ S}$ and $\mathbf{Y}_3$ are connected in parallel.

Calculate the equivalent admittance.

$$\begin{aligned}\mathbf{Y}_4 &= (j5) + \mathbf{Y}_3 \\ &= j5 + 0.4378 - j0.227 \\ &= 0.4378 + j4.773 \text{ S}\end{aligned}$$

Draw the modified circuit diagram.

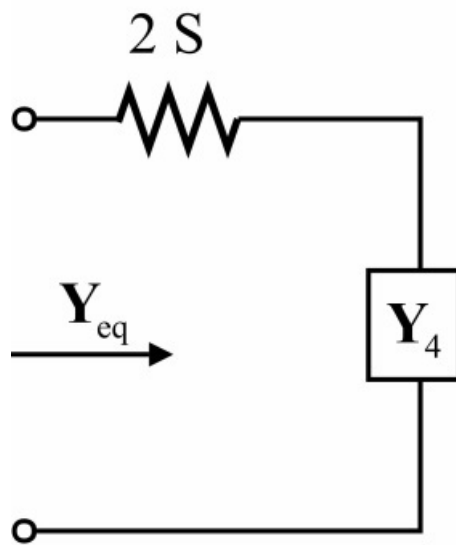


Figure 5

Step 8 of 8

From Figure 5, 2 S and $\mathbf{Y}_4$ are connected in series.

Calculate the equivalent admittance.

$$\begin{aligned}\frac{1}{\mathbf{Y}_{\text{eq}}} &= \frac{1}{2} + \frac{1}{\mathbf{Y}_4} \\ &= \frac{1}{2} + \frac{1}{0.4378 + j4.773} \\ &= 0.5 + 0.019 - j0.2 \\ &= 0.519 - j0.2\end{aligned}$$

$$\begin{aligned}\mathbf{Y}_{\text{eq}} &= \frac{1}{0.519 - j0.2} \\ &= 1.66 + j0.66 \text{ S}\end{aligned}$$

Thus, the equivalent admittance of the circuit is $\boxed{1.66 + j0.66 \text{ S}}$.