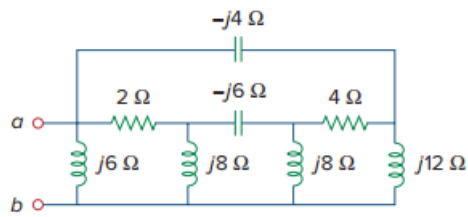


Problem

Determine the equivalent impedance of the circuit in Fig. 9.80.


Figure 9.80:



Step-by-step solution

Step 1 of 2

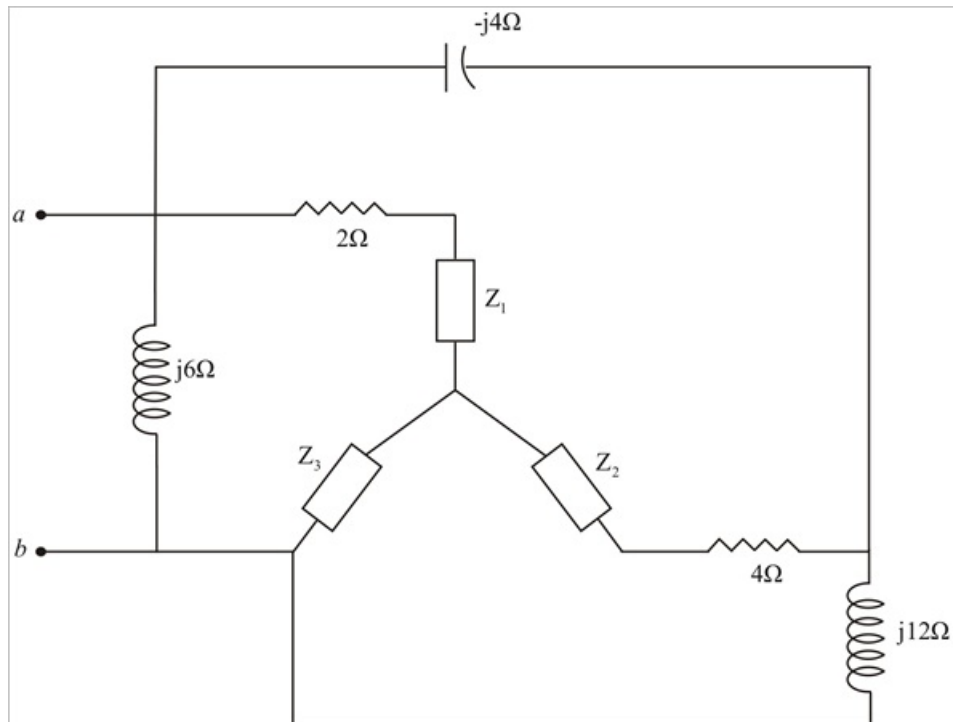Transform the delta connection to a WYE connector as in fig(a), & then transform the WYE connection to a delta connection as in fig(b).



Step 2 of 2

