


Problem

Design an RL circuit to provide a 90° leading phase shift.

Step-by-step solution

Step 1 of 2

One such RL circuit is shown below.

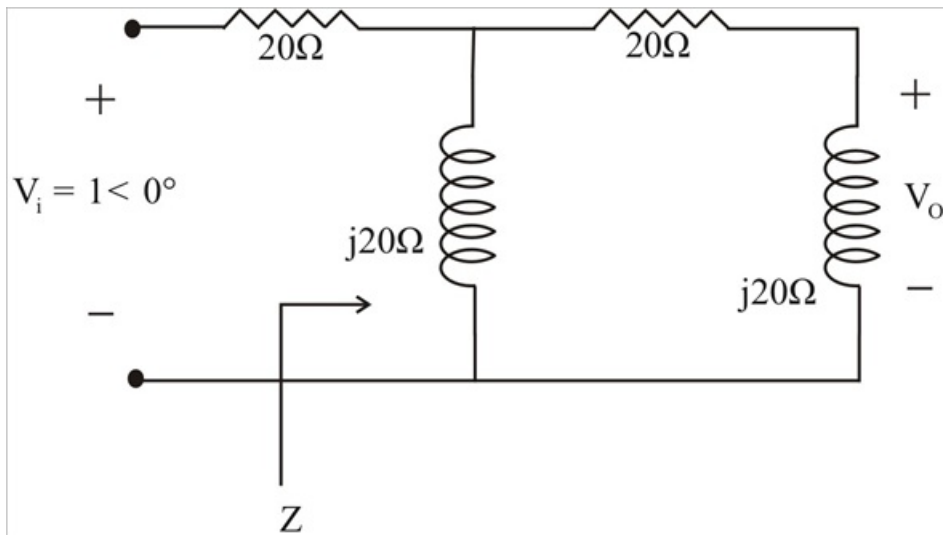

Step 2 of 2

We now want to show that this circuit will produce a 90° phase shift.

$$\begin{aligned}
 Z &= j20 \parallel (20 + j20) \\
 &= \frac{(j20)(20 + j20)}{20 + j40} = \frac{-20 + j20}{1 + j20} \\
 &= 4(1 + j3) \\
 V &= \frac{Z}{Z + 20} V_i = \frac{4 + j2}{24 + j12} (1 \angle 0^\circ) \\
 &= \frac{1 + j3}{6 + j3} = \frac{1}{3}(1 + j) \\
 V_o &= \frac{j20}{20 + j20} - V = \left(\frac{j}{1 + j} \right) \left(\frac{1}{3}(1 + j) \right) \\
 &= \frac{1}{3} = 0.3333 \angle 90^\circ .
 \end{aligned}$$

This shown that the output leads the input by 90° .