

Problem


Design a circuit that will transform a sinusoidal voltage input to a cosinusoidal voltage output.

Step-by-step solution

Step 1 of 1

Since $\cos(\omega t) = \sin(\omega t + 90^\circ)$, We need a phase shift circuit that will cause the output to lead the $\frac{1}{P}$ by 90° .

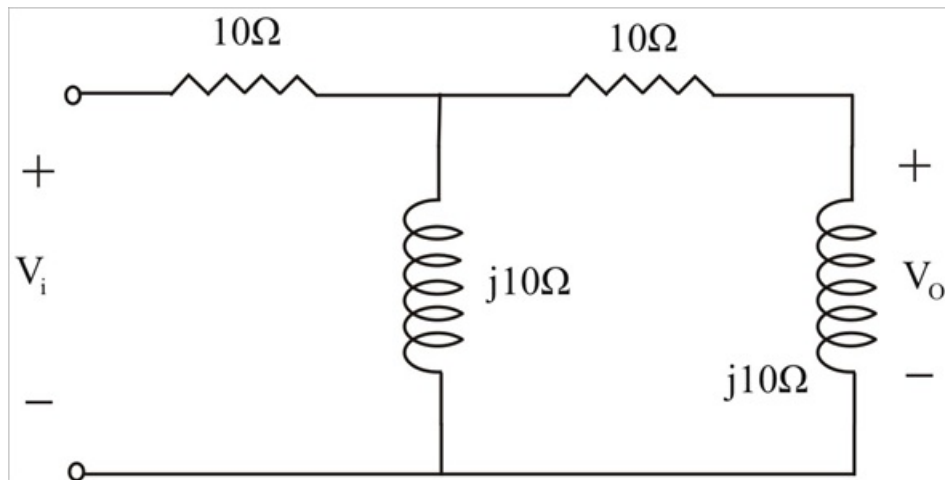This is achieved by the RLC circuit shown below, as explained in the previous problem.



This can also be obtained by an RC circuit.