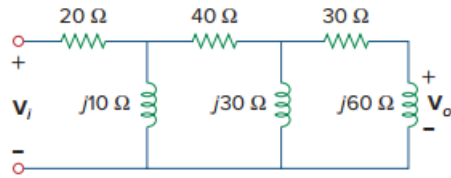


Problem

- (a) Calculate the phase shift of the circuit in Fig. 9.82.
- (b) State whether the phase shift is leading or lagging (output with respect to input).
- (c) Determine the magnitude of the output when the input is 120 V.


Figure 9.82:



Step-by-step solution

Step 1 of 5

(A) Consider the circuit shown.

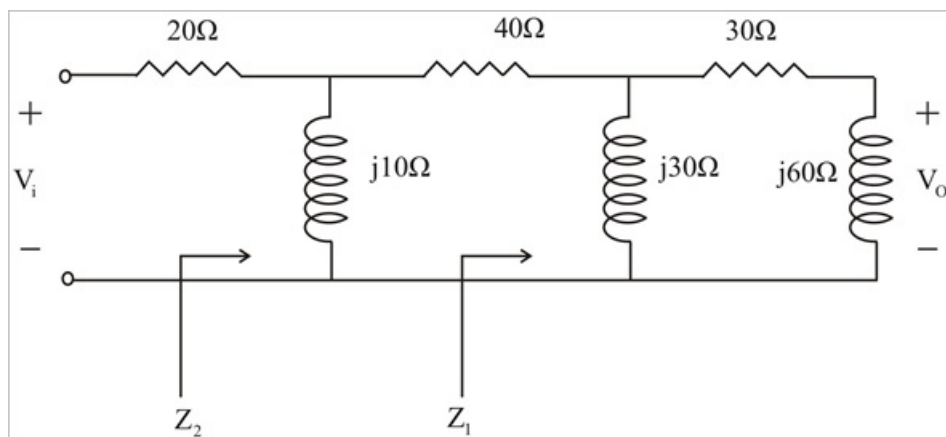

Step 2 of 5

$$Z_1 = j30 \parallel (30 + j60) = \frac{(j30)(30 + j60)}{30 + j90} = 3 + j21$$

$$Z_2 = j10 \parallel (40 + Z_1) = \frac{(j10)(43 + j21)}{43 + j31}$$

$$= 1.535 + j8.896 = 9.028 \angle 80.21^\circ$$

Let $V_1 = 1 \angle 0^\circ$

$$V_2 = \frac{Z_2}{Z_2 + 20} V_1 = \frac{(9.028 \angle 80.21^\circ)(1 \angle 0^\circ)}{21.535 + j8.896}$$

$$V_2 = 0.3875 \angle 57.77^\circ$$

$$V_1 = \frac{Z_1}{Z_1 + 40} V_2 = \frac{3 + j21}{43 + j21} V_2$$

Step 3 of 5

$$= \frac{(21.213 \angle 81.87^\circ)(0.3875 \angle 57.77^\circ)}{47.85 \angle 26.03^\circ}$$

$$V_1 = 0.1718 \angle 113.61^\circ$$

$$V_0 = \frac{j60}{30+j60}V_1 = \frac{j2}{1+j2}V_1 = \frac{2}{5}(2+j)V_1$$

$$V_0 = (0.8944 \angle 26.50^\circ)(0.1718 \angle 113.6^\circ)$$

$$V_0 = 0.1536 \angle 140.2^\circ$$

Therefore the phase shift is 140.2° .

Step 4 of 5

(B) The phase shift is leading.

Step 5 of 5

(C) If $V_1 = 120$ V, Then,

$$V_0 = (120)(0.1536 \angle 140.2^\circ)$$

$$= 18.43 \angle 140.2^\circ \text{ V}$$

And the magnitude is 18.43 V.