

Problem


Consider the phase-shifting circuit in Fig. 9.83. Let $V_i = 120$ V operating at 60 Hz. Find:

(a) V_o when R is maximum

(b) V_o when R is minimum

(c) the value of R that will produce a phase shift of 45°

Figure 9.83:

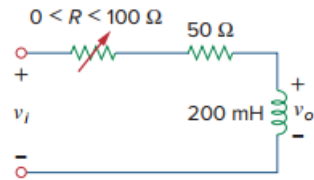

Step-by-step solution

Step 1 of 4

$$L = 200 \text{ mH}$$

$$j\omega L = j(2\pi)(60)(200 \times 10^{-3})$$

$$j\omega L = j75.4 \Omega$$

$$V_o = \frac{j75.4}{R + 50 + j75.4}$$

$$V_i = \frac{j75.4}{R + 50 + j75.4} (120 \angle 0^\circ)$$

Step 2 of 4

(a)

When $R = 100 \Omega$

$$V_o = \frac{j75.4}{150 + j75.4} (120 \angle 0^\circ)$$

$$V_o = \frac{(75.4 \angle 90^\circ)(120 \angle 0^\circ)}{167.88 \angle 26.69^\circ}$$

$$V_o = 53.89 \angle 63.31^\circ \text{ V}$$

Step 3 of 4

(b)

When $R = 0 \Omega$

$$V_0 = \frac{j75.4}{50 + j75.4} (120 \angle 0^\circ)$$

$$V_0 = \frac{(75.4 \angle 90^\circ)(120 \angle 0^\circ)}{90.47 \angle 56.45^\circ}$$

$$V_0 = 100 \angle 33.55^\circ \text{ V}$$

Step 4 of 4

(c)

To produce a phase shift of 45° .

The phase of $V_0 = 90^\circ + 0^\circ - \alpha = 45^\circ$.

Hence,

$$\alpha = \text{Phase of } (R + 50 + j75.4)$$

$$\alpha = 75^\circ$$

For α to be 45°

$$R + 50 = 75.4$$

Therefore,

$$R = 25.4 \Omega$$