

Chapter 9, Problem 82P

Problem

A capacitance bridge balances when $R_1 = 100\ \Omega$, $R_2 = 2\ \text{k}\Omega$, and $C_s = 40\ \mu\text{F}$. What is C_x , the capacitance of the capacitor under test?

Step-by-step solution

Step 1 of 1

$$\begin{aligned}C_x &= \left(\frac{R_1}{R_2}\right)C_s \\&= \left(\frac{100}{2000}\right) \times (40 \times 10^{-6}) \\&= 2\ \mu\text{F} .\end{aligned}$$