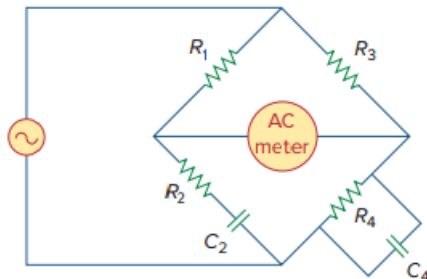


Problem

The ac bridge circuit of Fig. 9.85 is called a *Wien bridge*. It is used for measuring the frequency of a source. Show that when the bridge is balanced,

$$f = \frac{1}{2\pi\sqrt{R_2 R_4 C_2 C_4}}$$

Figure 9.85:



Step-by-step solution

Step 1 of 2

$$\text{Let } Z_1 = R_1, \quad Z_2 = R_2 + \frac{1}{j\omega C_2}, \quad Z_3 = R_3$$

$$\text{And } Z_4 = R_4 \parallel \frac{1}{j\omega C_4}$$

$$Z_4 = \frac{R_4}{j\omega R_4 C_4 + 1} = \frac{-j R_4}{\omega R_4 C_4 - j}$$

$$\text{Since, } Z_4 = \left(\frac{Z_3 Z_2}{Z_1} \right) \Rightarrow Z_1 Z_4 = Z_2 Z_3$$

$$\frac{-j R_4 R_1}{\omega R_4 C_4 - j} = R_3 \left(R_2 - \frac{j}{\omega C_2} \right)$$

$$\frac{-j R_4 R_1 (\omega R_4 C_4 + j)}{\omega^2 R_4^2 C_4^2 + 1} = R_3 R_2 - \frac{j R_3}{\omega C_2}$$

Step 2 of 2

Equating the real and imaginary components,

$$\frac{R_1 R_4}{\omega^2 R_4^2 C_4^2 + 1} = R_2 R_3 \rightarrow (1)$$

$$\left(\frac{\omega R_1 R_4^2 C_4}{\omega^2 R_4^2 C_4^2 + 1} \right) = \frac{R_3}{\omega C_2} \rightarrow (2)$$

Dividing (1) by (2),

$$\frac{1}{\omega R_4 C_4} = \omega R_2 C_2$$

$$\omega^2 = \frac{1}{R_2 C_2 R_4 C_4}$$

$$\omega^2 = 2\pi f = \frac{1}{\sqrt{R_2 C_2 R_4 C_4}}$$

$$f = \frac{1}{2\pi \sqrt{R_2 C_2 R_4 C_4}} .$$