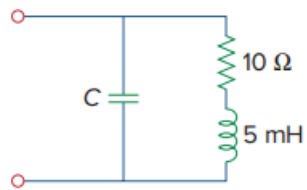


Problem

An industrial load is modeled as a series combination of an inductor and a resistance as shown in Fig. 9.89. Calculate the value of a capacitor C across the series combination so that the net impedance is resistive at a frequency of 2 kHz.

Figure 9.89:



Step-by-step solution

Step 1 of 4

Draw the circuit diagram as shown below.

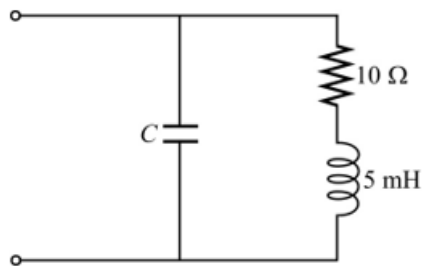


Figure 1

Step 2 of 4

Calculate the angular frequency.

$$\begin{aligned}\omega &= 2\pi f \\ &= (2)(3.14)(2 \times 10^3) \\ &= 12.566 \times 10^3 \text{ rad/s}\end{aligned}$$

Resistance $R = 10 \Omega$ and inductance $L = 5 \text{ mH}$.

Inductor, 5 mH is in series with the resistor 10Ω . The impedance combination is in parallel with the capacitor.

Given net impedance is resistive at a frequency of 2 kHz .

$$\begin{aligned}Z_{\text{eq}} \text{ or } Z_{\text{net impedance}} &= \frac{(R + j\omega L) \left(\frac{1}{j\omega C} \right)}{(R + j\omega L) + \frac{1}{j\omega C}} \\ &= \frac{R + j\omega L}{j\omega RC + j^2 \omega^2 LC + 1} \\ &= \frac{R + j\omega L}{(1 - \omega^2 LC) + j\omega RC} \times \frac{(1 - \omega^2 LC) - j\omega RC}{(1 - \omega^2 LC) - j\omega RC} \\ &= \frac{R(1 - \omega^2 LC) - j\omega R^2 C + j\omega L(1 - \omega^2 LC) + \omega^2 LRC}{(1 - \omega^2 LC)^2 + (\omega RC)^2}\end{aligned}$$

Step 3 of 4

Simplify further.

$$Z_{\text{eq}} \text{ or } Z_{\text{net impedance}} = \frac{R(1 - \omega^2 LC) + \omega^2 LRC + j(\omega L(1 - \omega^2 LC) - \omega R^2 C)}{(1 - \omega^2 LC)^2 + (\omega RC)^2}$$

The net impedance is resistive that means imaginary part is zero.

$$\begin{aligned}\frac{\omega L(1 - \omega^2 LC) - \omega R^2 C}{(1 - \omega^2 LC)^2 + (\omega RC)^2} &= 0 \\ \omega L(1 - \omega^2 LC) - \omega R^2 C &= 0 \\ \omega L - \omega^3 L^2 C &= \omega R^2 C \\ L - \omega^2 L^2 C &= R^2 C \\ C(R^2 + \omega^2 L^2) &= L\end{aligned}$$

Step 4 of 4

Simplify further.

$$C = \frac{L}{R^2 + \omega^2 L^2}$$

Substitute 10 for R , 5×10^{-3} for L and 12.566×10^3 for ω in the equation.

$$\begin{aligned}C &= \frac{5 \times 10^{-3}}{100 + (2\pi \times 2 \times 10^3)^2 (5 \times 10^{-3})^2} \\ &= 1.233 \times 10^{-6} \text{ F} \\ &= 1.233 \mu\text{F}\end{aligned}$$

Therefore, the value of capacitance C is $1.233 \mu\text{F}$.