

Problem

A transmission line has a series impedance of $\mathbf{Z} = 100/75^\circ \Omega$ and a shunt admittance of $\mathbf{Y} = 450/48^\circ \mu\text{S}$. Find: (a) the characteristic impedance $\mathbf{Z}_0 = \sqrt{\mathbf{Z}/\mathbf{Y}}$, (b) the propagation constant $\gamma = \sqrt{\mathbf{ZY}}$.

Step-by-step solution

Step 1 of 2

$$\begin{aligned} \text{(A) } \mathbf{Z}_0 &= \sqrt{\frac{\mathbf{Z}}{\mathbf{Y}}} \\ &= \sqrt{\frac{100 \angle 75^\circ}{450 \angle 48^\circ \times 10^{-6}}} \\ &= 471.4 \angle 135^\circ \Omega . \end{aligned}$$

Step 2 of 2

$$\begin{aligned} \text{(B) } \gamma &= \sqrt{\mathbf{ZY}} = \sqrt{\frac{100 \angle 75^\circ}{(450 \angle 48^\circ \times 10^{-6})^{-1}}} \\ \text{Or, } &= \sqrt{100 \angle 75^\circ \times 450 \angle 48^\circ \times 10^{-6}} \\ &= 0.2121 \angle 61.5^\circ . \end{aligned}$$