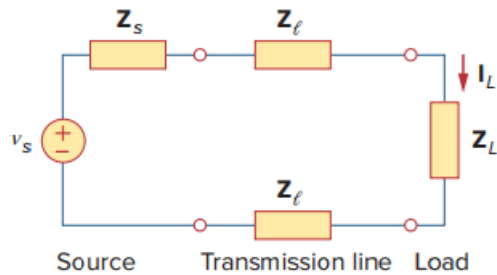


Problem

A power transmission system is modeled as shown in Fig. 9.92. Given the source voltage and circuit elements

$$\begin{aligned} \mathbf{V}_s &= 115 \angle 0^\circ \text{ V,} && \text{source impedance} \\ \mathbf{Z}_s &= (1 + j0.5) \, \Omega, && \text{line impedance} \\ \mathbf{Z}_l &= (0.4 + j0.3) \, \Omega, && \text{and load impedance} \\ \mathbf{Z}_L &= (23.2 + j18.9) \, \Omega, && \text{find the load current } \mathbf{I}_L. \end{aligned}$$

Figure 9.92:



Step-by-step solution

Step 1 of 1

$$\begin{aligned} Z &= Z_a + 2Z_b + Z_L \\ Z &= (1 + 0.8 + 23.2) + j(0.5 + 0.6 + 18.9) \\ Z &= 25 + j20 \\ I_L &= \frac{V_s}{Z} = \frac{115 \angle 0^\circ}{32.02 \angle 38.66^\circ} \\ I_L &= 3.592 \angle -38.66^\circ \text{ A} \quad \text{Answer} \end{aligned}$$