

2023-2024
2nd year /Electronic I
Electronic and Telecommunication Department.
Engineering Science/ Kufa University

The Field-Effect Transistor

Constant-Current Biasing:

Example 3.3: Determine the currents and voltages in a MOSFET constant-current source. For the circuit shown in Figure 3.3, the transistor parameters are: $K_{n1} = 0.2 \text{ mA/V}^2$, $K_{n2} = K_{n3} = K_{n4} = 0.1 \text{ mA/V}^2$, and $V_{TN1} = V_{TN2} = V_{TN3} = V_{TN4} = 1 \text{ V}$.

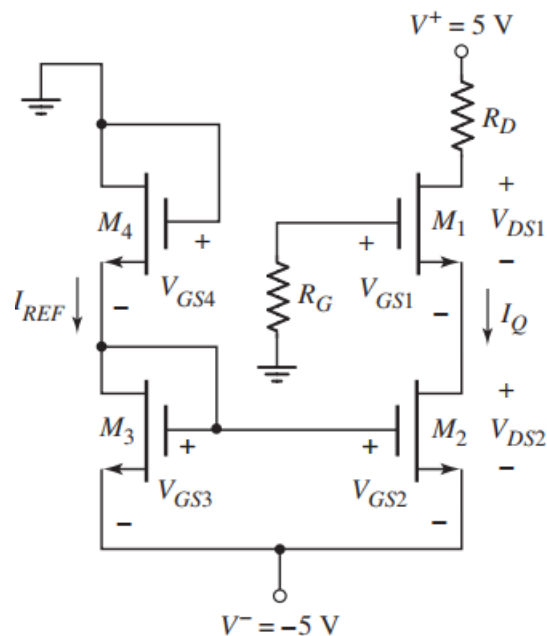


Figure 3.3 Implementation of a MOSFET constant-current source

Solution: Step 1 V_{GS3}

Since the reference current is the same in transistors M3 and M4, then

$$K_{n3}(V_{GS3} - V_{TN3})^2 = K_{n4}(V_{GS4} - V_{TN4})^2$$

$$V_{GS4} = V_{GS3} = -V_{DD}$$

This yields to $V_{GS3} = 2.5 \text{ V}$ which is equal to V_{GS4}

Step 2 I_Q

Since M_3 and M_4 are identical transistors, V_{GS3} should be one-half of the bias voltage. The bias current I_Q is then

$$I_Q = (0.1) \cdot (2.5 - 1)^2 = 0.225 \text{ mA}$$

Step 3 V_{GS1}

The gate-to-source voltage on M1 is found from

$$I_Q = K_{n1}(V_{GS1} - V_{TN1})^2$$

$$0.225 = (0.2) \cdot (V_{GS1} - 1)^2$$

which yields

$$V_{GS1} = 2.06 \text{ V}$$

Step 4 V_{DS2}

The drain-to-source voltage on M2 is

$$V_{DS2} = (-V_{DD}) - V_{GS1} = 5 - 2.06 = 2.94 \text{ V}$$

Since $V_{DS2} = 2.94 \text{ V} > V_{DS}(\text{sat}) = V_{GS2} - V_{TN2} = 2.5 - 1 = 1.5 \text{ V}$, M_2 is biased in the saturation region.

Multistage MOSFET Circuits

Cascade Configuration

Example 3.3: Design the biasing of a multistage MOSFET circuit to meet specific requirements. Consider the circuit shown in Figure 3.6 with transistor parameters $K_{n1} = 500 \mu\text{A}/\text{V}^2$, $K_{n2} = 200 \mu\text{A}/\text{V}^2$, $V_{TN1} = V_{TN2} = 1.2 \text{ V}$, and $\lambda_1 = \lambda_2 = 0$. Design the circuit such that $I_{DQ1} = 0.2 \text{ mA}$, $I_{DQ2} = 0.5 \text{ mA}$, $V_{DSQ1} = V_{DSQ2} = 6 \text{ V}$, and $R_i = 100 \text{ k}\Omega$. Let $R_{Si} = 4 \text{ k}\Omega$.

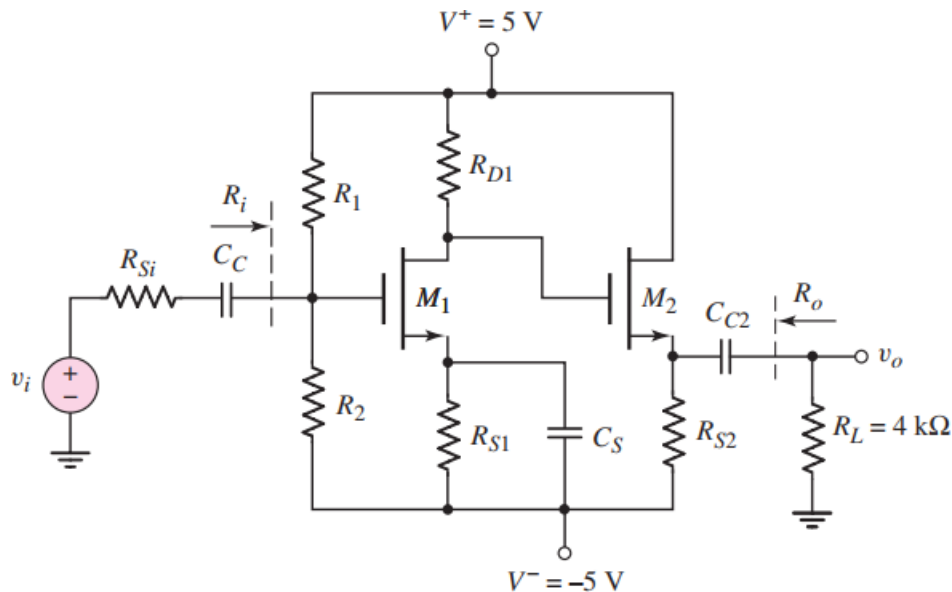


Figure 3.6 Common-source amplifier in cascade with source follower

Solution:

Step 1 R_{S2}

For output transistor M_2 , we have

$$V_{DSQ2} = 5 - (-5) - I_{DQ2} R_{S2}$$

$$\text{or } 6 = 10 - (0.5) R_{S2}$$

which yields $R_{S2} = 8 \text{ k}\Omega$.

Step 2 R_{D1}

Assuming transistors are biased in the saturation region and the value of K_{GS2}

$$I_{DQ2} = K_{n2}(V_{GS2} - V_{TN2})^2$$

$$\text{or } 0.5 = 0.2(V_{GS2} - 1.2)^2$$

which yields $V_{GS2} = 2.78 \text{ V}$

Since $V_{DSQ2} = 6 \text{ V}$, the source voltage of M_2 is $V_{S2} = -1 \text{ V}$. With $V_{GS2} = 2.78 \text{ V}$, the gate voltage on M_2 must be

$$V_{G2} = -1 + 2.78 = 1.78 \text{ V}$$

$$R_{D1} = [5 - 1.78] / 0.2 = 16.1 \text{ k}\Omega$$

Step 3 R_{S1} is then

For $V_{DSQ1} = 6 \text{ V}$, the source voltage of M_1 is

$$V_{S1} = 1.78 - 6 = -4.22 \text{ V}$$

$$R_{S1} = [-4.22 - (-5)] / 0.2 = 3.9 \text{ k}\Omega.$$

Step 4 R_1 and R_2

For transistor M_1 , we have

$$I_{DQ1} = K_{n1}(V_{GS1} - V_{TN1})^2$$

$$\text{or } 0.2 = 0.50(V_{GS1} - 1.2)^2$$

which yields $V_{GS1} = 1.83 \text{ V}$

To find R_1 and R_2 , we can write

$$V_{GS1} = \left(\frac{R_2}{R_1 + R_2} \right) (10) - I_{DQ1} R_{S1}$$

$$\frac{R_2}{R_1 + R_2} = \frac{1}{R_1} \cdot \left(\frac{R_1 R_2}{R_1 + R_2} \right) = \frac{1}{R_1} \cdot R_i$$

then, since the input resistance is specified to be 100 k, we have

$$1.83 = \frac{1}{R_1}(100)(10) - (0.2)(3.9)$$

which yields $R_1 = 383 \text{ k}\Omega$. From $R_i = 100 \text{ k}\Omega$, we find that $R_2 = 135 \text{ k}\Omega$.

Example 3.4: Design the biasing of the cascode circuit to meet specific requirements. For the circuit shown in Figure 3.7, the transistor parameters are: $V_{TN1} = V_{TN2} = 1.2 \text{ V}$, $K_{n1} = K_{n2} = 0.8 \text{ mA/V}^2$, and $\lambda_1 = \lambda_2 = 0$. Let $R_1 + R_2 + R_3 = 300 \text{ k}\Omega$ and $R_S = 10 \text{ k}\Omega$. Design the circuit such that $I_{DQ} = 0.4 \text{ mA}$ and $V_{DSQ1} = V_{DSQ2} = 2.5 \text{ V}$.

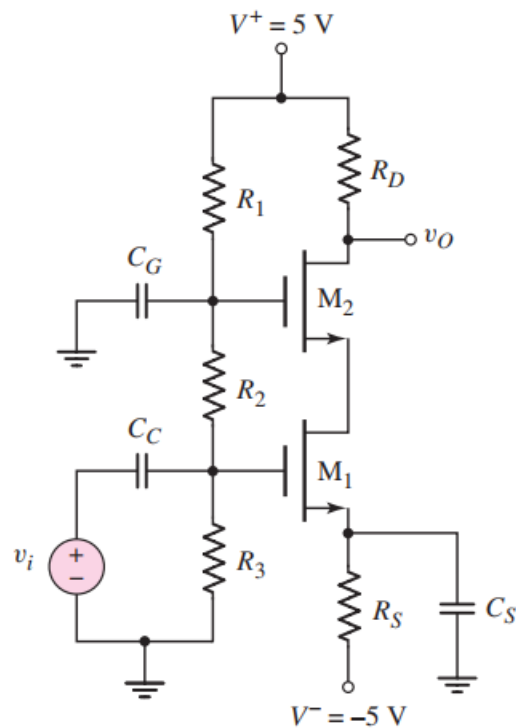


Figure 3.7 NMOS cascode circuit

Solution:

Step 1 R_3

The dc voltage at the source of M_1 is

$$V_{S1} = I_{DQ} R_S - 5 = (0.4)(10) - 5 = -1V$$

Since M_1 and M_2 are identical transistors, and since the same current exists in the two transistors, the gate-to-source voltage is the same for both devices. We have

$$I_D = K_n (V_{GS} - V_{TN})^2$$

or

$$0.4 = 0.8(V_{GS} - 1.2)^2$$

which yields

$$V_{GS} = 1.907 \text{ V}$$

Then,

$$V_{G1} = \left(\frac{R_3}{R_1 + R_2 + R_3} \right) (5) = V_{GS} + V_{S1}$$

$$\left(\frac{R_3}{300} \right) (5) = 1.907 - 1 = 0.907$$

which yields

$$R_3 = 54.4 \text{ k}\Omega.$$

Step 2 R_2

The voltage at the source of M_2 is

$$V_{S2} = V_{DSQ1} + V_{S1} = 2.5 - 1 = 1.5 \text{ V}$$

Then,

$$V_{G2} = \left(\frac{R_2 + R_3}{R_1 + R_2 + R_3} \right) (5) = V_{GS} + V_{S2}$$

$$\left(\frac{R_2 + R_3}{300} \right) (5) = 1.907 + 1.5 = 3.407 \text{ V}$$

which yields

$$R_2 + R_3 = 204.4 \text{ k}\Omega$$

and

$$R_2 = 150 \text{ k}\Omega$$

Step 3 R_1

Therefore

$$R_1 = 95.6 \text{ k}\Omega$$

Step 4 R_D

The voltage at the drain of M_2 is

$$V_{D2} = V_{DSQ2} + V_{S2} = 2.5 + 1.5 = 4 \text{ V}$$

The drain resistor is therefore

$$R_D = \frac{5 - V_{D2}}{I_{DQ}} = \frac{5 - 4}{0.4} = 2.5 \text{ k}\Omega$$

Note: Since $V_{DS} = 2.5 \text{ V} > V_{GS} - V_{TN} = 1.91 - 1.2 = 0.71 \text{ V}$, each transistor is biased in the saturation region.